

# Lecture 17

EE 421 / CS 425

## Digital System Design

Fall 2025

Shahid Masud

# Topics

- Examples: **Online tools for Binary Multiplication**
- Binary Divider Operation
- Binary Divider Circuit
- STG of Divider
- Floating Point Representation (if time permits)
- Floating Point Multiplier – design and operation

<http://www.ecs.umass.edu/ece/koren/arith/simulator/Booth/>

<http://www.ecs.umass.edu/ece/koren/>

Many simulators of Computer Arithmetic are available:

<http://www.ecs.umass.edu/ece/koren/arith/simulator/>



# Online Modified Booth (Radix 4) Encoding

<http://www.ecs.umass.edu/ece/koren/arith/simulator/ModBooth/>

Simulator available on Prof Koren's website

# Delay computation in binary array multiplier

Previous topic:

Delay computation in Array Multiplier (binary inputs):


<http://www.ecs.umass.edu/ece/koren/arith/simulator/ArrMlt/>

# Radix 4 Coding for Multiplication

$m_{i+1}$	$m_i$	$m_{i-1}$	Code	Multiply Actions
0	0	0	0	Shift Left by 2
0	0	1	1	Add Multiplicand, Shift Left by 2
0	1	0	2	Add Multiplicand, Shift Left by 2
0	1	1	3	Shift by 1, Add Multiplicand, Shift by 1
1	0	0	4	Shift by 1, Subtract Multiplicand, Shift by 1
1	0	1	5	Subtract Multiplicand, Shift Left by 2
1	1	0	6	Subtract Multiplicand, Shift Left by 2
1	1	1	7	Shift Left by 2


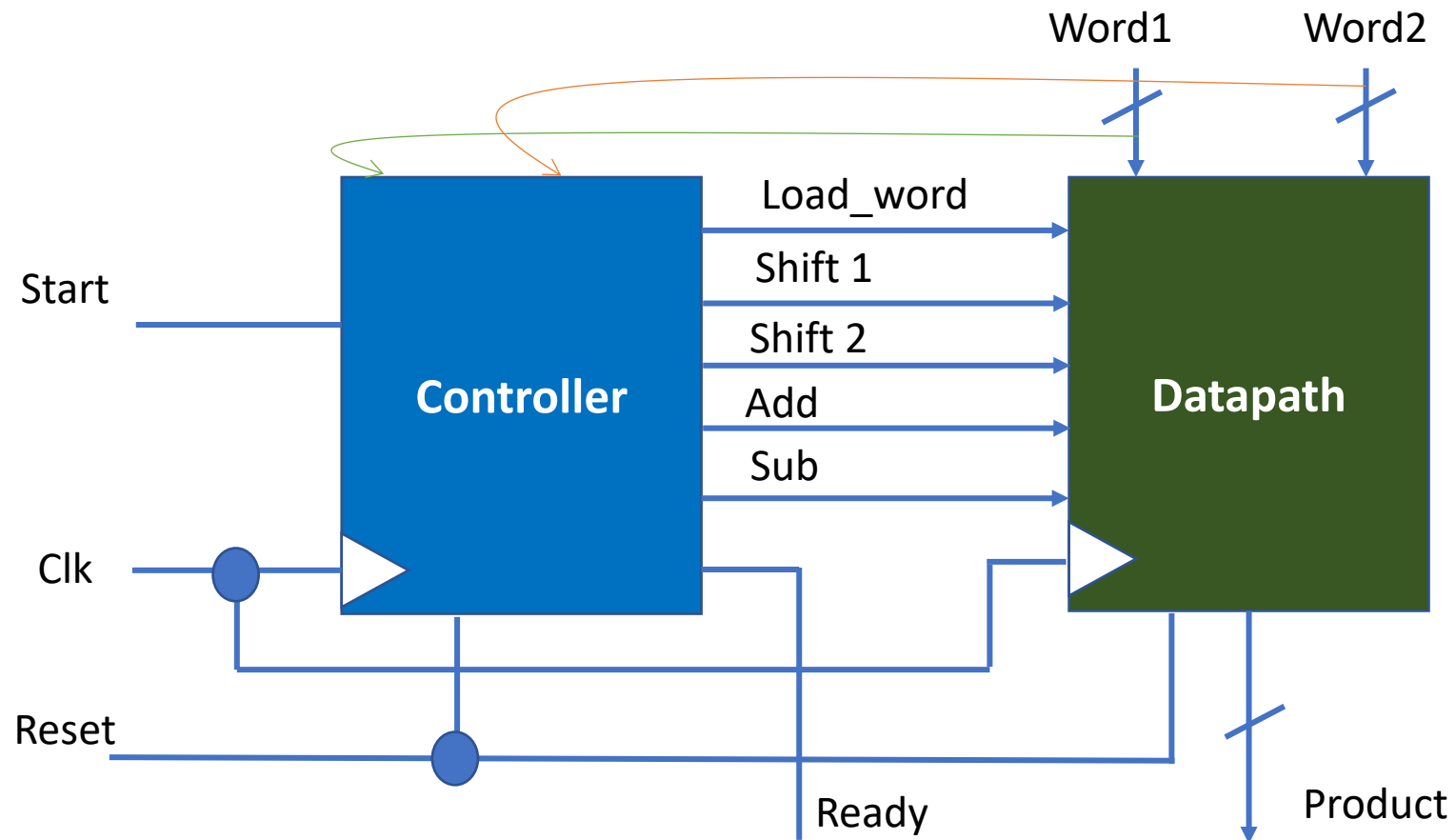
# Data Path Architecture of a Radix 4 Sequential Multiplier





# Radix 4 Multiplication – Example 3

Show Radix 4 Encoded multiplication of **76 x 55**, using 8 bits for both numbers

76 = 0100 1100  
And 2's Compl is  
-76 = 1011 0100

55 = 0011 0111  
And 2's Compl is  
-55 = 1100 1001

Convert 55 = 0011 0111 to Radix 4 Encoded bits

55 = 0 0 1 1 0 1 1 1 [0]

Imagine Zero

**RECODED**  
110 → 0-1  
011 → 10  
110 → 0-1  
001 → 01

76 = Multiplicand

X 55 = Recoded Multiplier

Partial Sum

Partial Sum

Result

										0	1	0	0	1	1	0	0
										0	1	0	-1	1	0	0	-1
	1	1	1	1	1	1	1	1	1	0	1	1	0	1	0	0	
	0	0	0	0	0	0	0	1	0	0	1	1	0	0	X	X	X
Partial Sum	0	0	0	0	0	0	0	1	0	0	0	0	1	0	1	0	0
	1	1	1	1	1	1	0	1	1	0	1	0	0	X	X	X	X
Partial Sum	1	1	1	1	1	1	1	0	1	0	1	0	1	0	1	0	0
	0	0	0	0	1	0	0	1	1	0	0	X	X	X	X	X	X
Result	0	0	0	0	1	0	0	0	0	0	1	0	1	0	1	0	0

0 -1 = Sub, Shl2

1 0 = Shl1, Add, Shl1

0 -1 = Sub, Shl2

0 1 = Add, Shl2

**Answer = 0001 0000 0101 0100 = (4+16+64+4096) = (4180)<sub>10</sub>**

# Division Operation in Hardware

# Division Operation in Decimal Numbers

Division of  $274 \div 13$

				2	1	Quotient
Divisor	1	3	2	7	4	Dividend
		-	-2	6		
				1	4	
			-	1	3	
		Remainder		1	Rem	

# Division Operation in Decimal Numbers

Division of  $299 \div 15$

			1	9	Quotient	
Divisor	1	5	2	9	9	Dividend
		-	2	8	5	
		Remainder	1	4	Rem	

# Decimal Division – another example

		1	0	0	4	Quotient
Divisor	8	8	0	3	5	Dividend
	-	8				
		0	0	3	5	
		-		3	2	
	Remainder				3	

### Division of $274 \div 13$

			2	1	
1	3	2	7	4	
	-	-2	6		
			1	4	
		-	1	3	
				1	Rem

## Divisor

Handwritten long division of 1101 by 101:

Divisor														
1	1	0	1	1	0	0	0	1	0	0	1	0	Dividend	
		-		0	1	1	0	1						
					1	0	0	0	0					
						-		1	1	0	1			
							0	0	0	1	1	1	0	
								-		1	1	0	1	
									0	0	0	1	Re	

## Remainder

# Division Operation in Binary – Example 2

Division of  $299 \div 15$

			1	9	
1	5	2	9	9	
	-	2	8	5	
			1	4	Rem


Divisor														Quotient			
1	1	1	1	1	0	0	1	0	1	0	1	1	Dividend				
				-	1	1	1	1									
					0	0	1	1	1	0	1						
				-	0	0	1	1	1	1	1						
					0	0	1	1	1	0	1						
									1	1	1	1					

# Division Operation in Binary – Example 3

								Quotient			
Divisor	1	0	1	1	1	0	0	1	0	0	1
				-	1	0	1	1			
					0	1	1	1	0		
				-		1	0	1	1		
					0	0	1	1	1	1	
				-			1	0	1	1	
					Remainder		0	1	0	0	Re



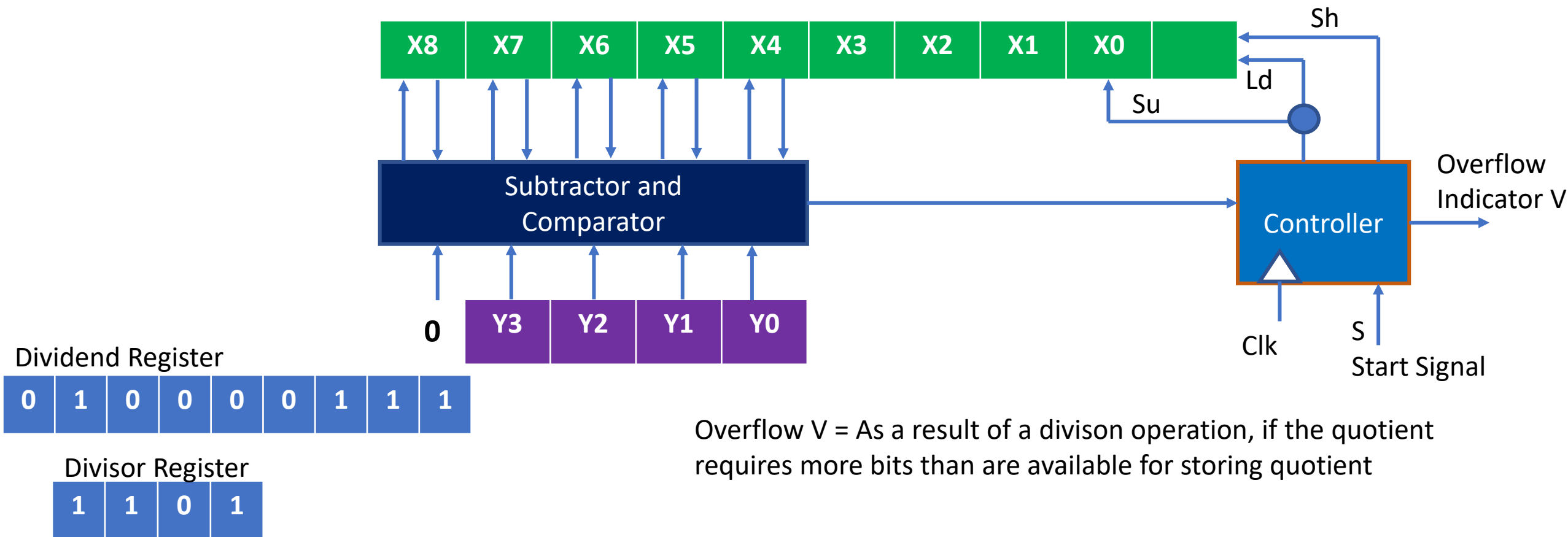
# Block Diagram of Sequential Binary Divider



# Operation of Sequential Binary Divider

Show binary division

135 ÷ 13

 

Dividend

1 0 0 0 0 1 1 1 0

1 1 0 1 Divisor

Dividing line between Dividend and Quotient

After the shift, the right most position in dividend register is 'empty'

Subtraction is now carried out. The first quotient digit of 1 is stored in the unused portion of the dividend register

0 0 0 1 1 1 1 1 1

First quotient digit

Next we shift the dividend one place to the left

0 0 1 1 1 1 1 1 0

1 1 0 1

Since subtraction yields negative result so we shift dividend to the left again, and the second quotient bit remains 0

0 1 1 1 1 1 1 0 0

1 1 0 1

Subtraction is now carried out, the third quotient digit of 1 is stored in the unused portion of the dividend register

0 0 0 1 0 1 1 0 1


Third quotient digit

A final shift is done and fourth quotient bit is set to 0

0 0 1 0 1 1 0 1 0

Quotient

# STG of a Binary Divider

 

**Su = Subtract Signal**

**C = Comparator Output**

**If divisor is greater than 5 leftmost dividend bits (as per given number),  
then C=0; otherwise C=1**

**Whenever C=1, then subtract signal is generated and quotient bit is set to 1**

**Whenever C=0, then subtraction cannot occur without a negative result so a  
Shift signal Sh is generated**

# Division Examples

- Try using 2's Complement Add instead of Sub in Division operations

# Floating Point Operations in Hardware

# Floating Point Arithmetic – Digital Design


$$N = (-1)^S \times (1+F) \times 2^E$$

E.g.  $91.820734 \times 10^{-34}$


- ❖ A signed-magnitude system for the fractional part and a biased notation for the exponent
- ❖ Three subfields
  - ❖ Sign S
  - ❖ Fraction F (or Significand or Mantissa)
  - ❖ Exponent E
- ❖ Sign bit is 0 for positive numbers, 1 for negative numbers
- ❖ Fractions always start from **1**.xxxx, hence the integer **1** is not written (register has xxxx)
- ❖ Exponent is biased by +127 (add 127 to whatever is in register bits)
- ❖ Normalize: Express numbers in the standard format by shifting of bits and adding / subtracting from Exponent register

# IEEE 754 Floating Point Representation

Single Precision IEEE 754

 

Double Precision IEEE 754

 

# Examples of Floating Point Representation

$-(13.45)_{10}$   
 $= (1101.01\ 1100\ 1100\ 1100\ \dots)^2$ ; this is un-normalized  
 $= (1.10101\ 1100\ 1100\ 1100\ 1100\ 1) \times 2^3$ ; normalized  
 Fraction part is 10101 1100 1100 1100 1  
 Biased Exponent is  $3+127 = 130$   
 Sign = 1

5.0345  
 $= 101.0000\ 1000\ 1101\ 0100\ 1111\ 110$ ; this is un-normalized  
 $= 1.01\ 0000\ 1000\ 1101\ 0100\ 1111\ 110 \times 2^2$ ; normalized  
 Biased Exponent =  $2+127 = 129 = (1000\ 0001)_2$   
 Fraction = 01 0000 1000 1101 0100 1111 110  
 Sign = 0



# Floating Point Multiplication

Consider two floating point numbers:  
 $(F_1 \times 2^{E1})$  and  $(F_2 \times 2^{E2})$

The product of these two numbers is:  
 $= (F_1 \times 2^{E1}) \times (F_2 \times 2^{E2})$   
 $= (F_1 \times F_2) \times 2^{(E1+E2)}$   
 $= F \times 2^E$

Sign of result depends on Sign of the two numbers

# Floating Point Multiplication Steps

1. **Normalize** the two numbers if not done already
2. The **exponents** of the **Multiplier** (E1) and the **multiplicand** (E2) bits are **added** and the base value is **subtracted** from the added result; The subtracted result is put in the exponential field of the result block  $\rightarrow E1+E2-\text{bias}$
3. **Multiply** the two fractions (or significands)
4. S1, the signed bit of the multiplicand is XOR'd with the multiplier signed bit of S2. The result is put into the resultant sign bit.
5. The **mantissa** of the Multiplier (M1) and multiplicand (M2) are **multiplied** and the result is placed in the resultant field of the mantissa (truncate/round the result for 24 bits)  $\rightarrow M1 * M2$
6. If the product is 0, adjust the proper representation of answer to 0
7. If the product fraction is too big, **Normalize** by shifting it right and incrementing the exponent
8. If the product fraction is too small, **Normalize** by shifting left and decrementing the exponent
9. Round to appropriate number of bits. If rounding results in loss of Normalization, then first **Normalize** and then do the rounding
10. If an exponent underflow (below -127) or overflow (above +127) occurs then generate an error condition

# Bit-widths required

- Multiply the mantissa values including the hidden (**guard**) bits in rounding register. The resultant product of the 24 bits mantissas (M1 and M2) is 48 bits (2 bits are to the left of binary point)
- 8 bit adder (subtractor) needed for Exponent

# Floating Point Multiplier Block Diagram - Example

## Definitions:

**St:** Start of Floating Point multiplication operation

**Mdone:** Fraction multiplication is complete

**FZ:** Fraction is Zero

**FV:** Fraction overflow (too small or too big)

**Fnorm:** F is normalized

**EV:** Exponent overflow

**Load:** Load F1, E1, F2, E2 into respective registers

**Adx:** Add Exponent; also start of multiplication


**SM8:** Set exponent to -8 to handle special case of 0

**RSF:** Shift fraction right; also increment E


**LSF:** Shift fraction left; also decrement E

**V:** overflow indicator

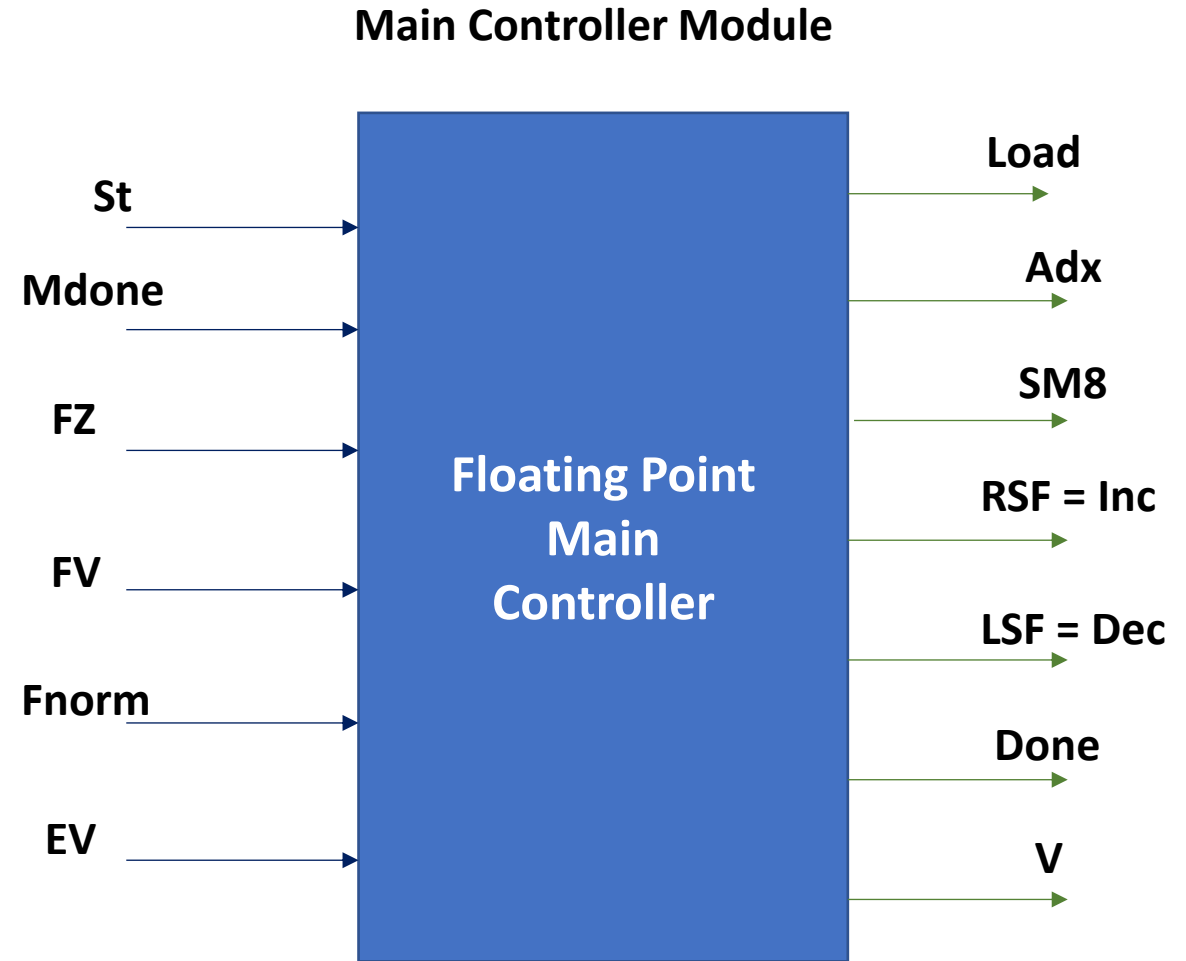**Done:** Floating Point multiplication is complete



# Data Path of Floating Point Multiplier

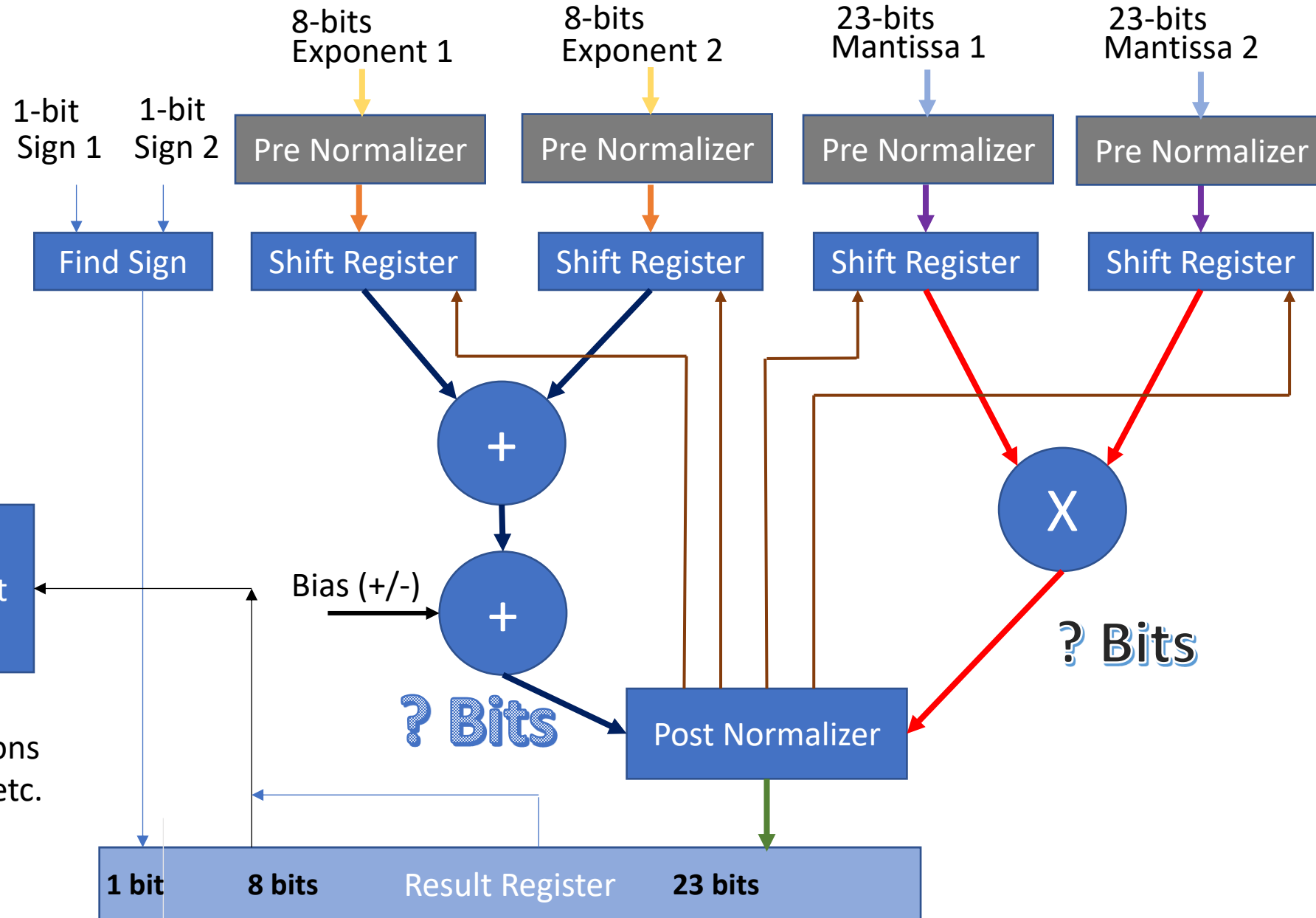

# Floating Point with Booth Multiplier



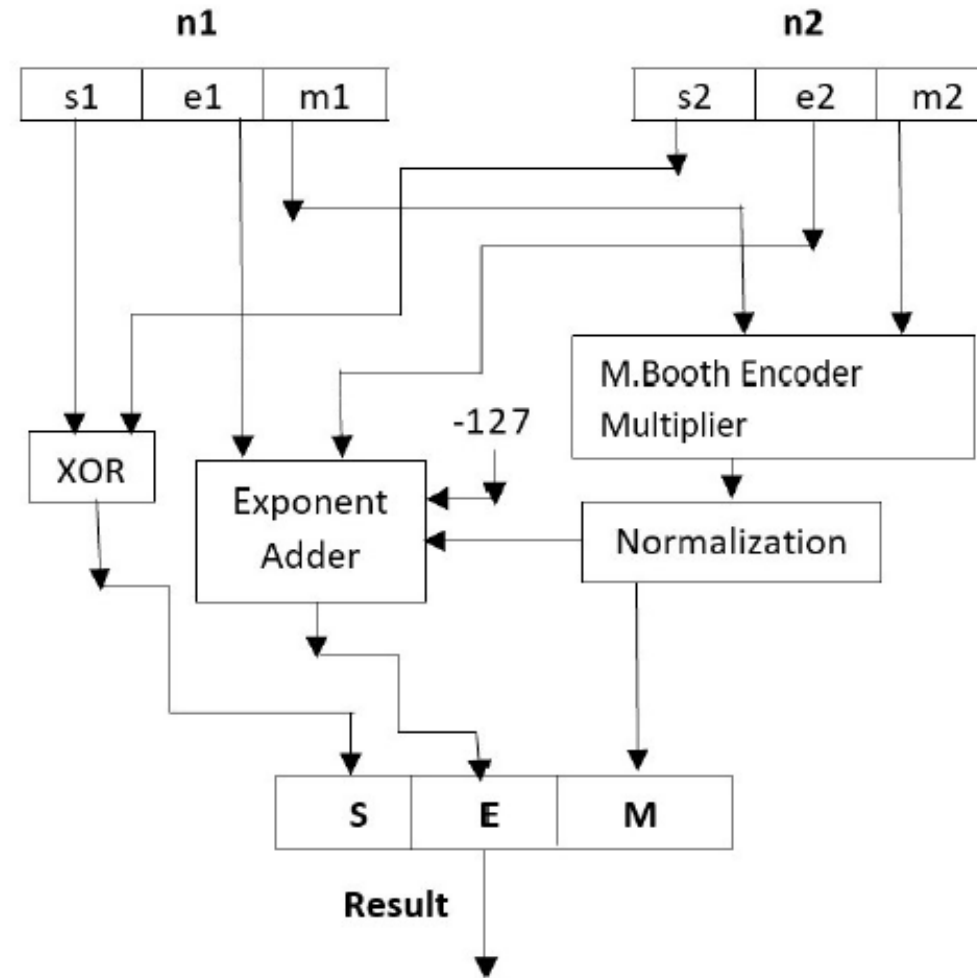


Fig. 4. Floating point Multiplication Block Diagram

# Identifying Pipeline Cuts

 

# Pipelined Floating Point Architecture

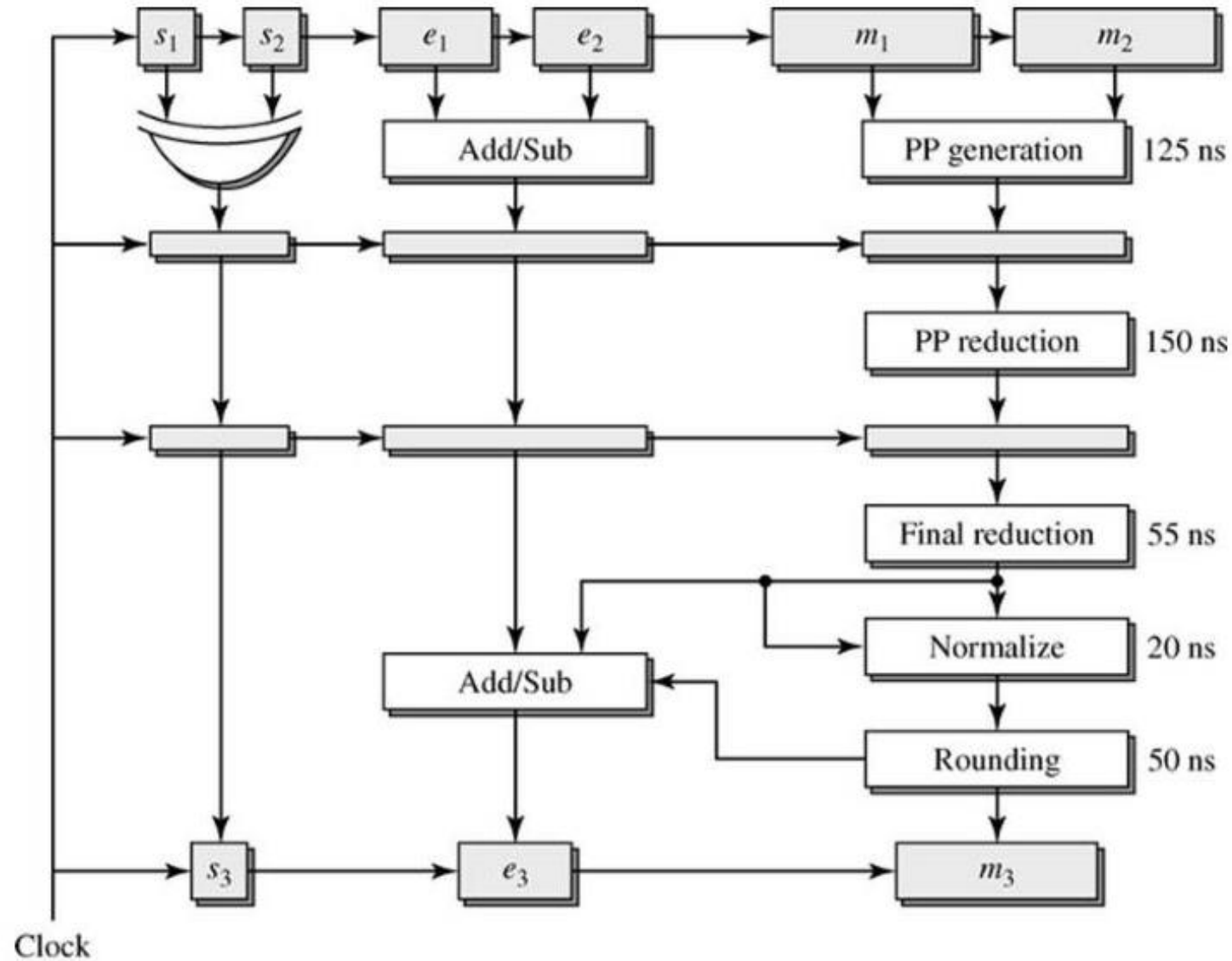



# Operation Details of Datapath

**Pre Normalize Block for Adder and Subtractor :** Calculate the difference between the smaller and larger exponent. Adjust the smaller fraction by right shifting it, determine if the operation is an add or subtract after resolving the sign bits. Check for NaNs on inputs.

**Pre Normalize Block for Multiplication:** Computes the sum/difference of exponents, checks for exponent overflow, underflow condition and INF value on an input.

**Post Normalize and Round Unit -** Normalize fraction and exponent. Also do all the roundings in parallel and then pick the output corresponding to the chosen rounding mode.

**Exceptions Unit** – This unit Generates the exception signals like sNaN, qNaN, Inf and Ine The IEEE standard defines two classes of NaNs(non numbers): i. quiet NaNs (qNaNs) : A qNaN is a NaN with the most significant fraction bit set. ii. signaling NaNs (sNaNs): A sNaN is a NaN with the most significant fraction bit clear.

The single precision floating point format is divided into three main parts corresponding to the sign , exponent and mantissa.

Multiplication of the two operands is done in three parts and thereby obtaining the Product.

The first part of the product which is the sign is determined by an exclusive OR function of the two input signs.

The exponent of the product which is the second part is calculated by adding the two input exponents. The third part which is the significand of the product is determined by multiplying the two input significands each with a '1' concatenated to it.

33

A multiplication of two floating-point numbers is done in four steps: • non-signed multiplication of mantissas: it must take account of the integer part, implicit in normalization. The number of bits of the result is twice the size of the operands (48 bits). • normalization of the result, the exponent can be modified accordingly . • addition of the exponents, taking into account the bias. • calculation of the sign.