

# Lecture 25

## EE 421 / CS 425

### Digital System Design

Fall 2025

Shahid Masud

# Topics

## QUIZ 5 TODAY

- Data **Scramblers**
- Data **Un-Scramblers**
- Scrambler Applications
- Scrambler Examples
- Binary Rate Multipliers – Maybe next lecture

# Rescheduled Lectures



- Rescheduled lecture: Academic Block SS Auditorium has been reserved for Make-up Class of EE 421 from

**10:00 AM to 11:30 AM on Saturday, 6th December 2025.**

- As per RO's below email, Academic Block-SS Auditorium has been reserved for reserved class of EE 421L/CS 425L on

**Monday, 8th December 2025 from 2:00 PM to 4:50 PM.**

- Details will be announced
- **Quiz 6 in Last lecture**

# What is a Scrambler?

- Scramblers → circuits that pseudo-randomly change the values of some bits in a data stream with the purpose of 'whitening' its spectrum to dilute strong spectral components.
- This will reduce electromagnetic interference and introduce data security as part of an encryption algorithm.
- In natural signals, e.g. voice, image, transducer, energy is concentrated in some bands. Scrambling → spread the energy to reduce interference and spikes.
- An ALFSR forms backbone of scrambling operation.
- There are two main types:
  - Additive Scrambler
  - Multiplicative Scrambler

# Example Applications of LFSR

Ref: from Wikipedia page

Digital broadcasting systems that use linear-feedback registers:

- [ATSC Standards](#) (digital TV transmission system – North America)
- [DAB](#) ([Digital Audio Broadcasting](#) system – for radio)
- [DVB-T](#) (digital TV transmission system – Europe, Australia, parts of Asia)
- [NICAM](#) (digital audio system for television)

Other digital communications systems using LFSRs:

- [INTELSAT](#) business service (IBS)
- Intermediate data rate (IDR)
- [HDMI 2.0](#)
- [SDI](#) (Serial Digital Interface transmission)
- Data transfer over [PSTN](#) (according to the [ITU-T](#) V-series recommendations)
- [CDMA](#) (Code Division Multiple Access) cellular telephony
- [100BASE-T2 "fast" Ethernet](#) scrambles bits using an LFSR
- [1000BASE-T Ethernet](#), the most common form of Gigabit Ethernet, scrambles bits using an LFSR
- [PCI Express](#)
- [SATA](#)<sup>[13]</sup>
- Serial attached SCSI (SAS/SPL)
- [USB 3.0](#)
- [IEEE 802.11a](#) scrambles bits using an LFSR
- [Bluetooth Low Energy](#) Link Layer is making use of LFSR (referred to as whitening)
- [Satellite navigation systems](#) such as [GPS](#) and [GLONASS](#). All current systems use LFSR outputs to generate some or all of their ranging codes (as the chipping code for CDMA or DSSS) or to modulate the carrier without data (like GPS L2 CL ranging code). GLONASS also uses [frequency-division multiple access](#) combined with DSSS.


**Other uses** [ [edit](#) ]

# Types of Scramblers

Standard	Scrambler type
V.34 (33 Kbps Modem)	Multiplicative
56 Kbps Modem	Multiplicative
DVB	Additive
LTE	Additive
IEEE 802.11 a	Additive
IEEE 802.16 a	Multiplicative


$1+x^4+X^7$  is polynomial for 802.11

# Typical Communication System

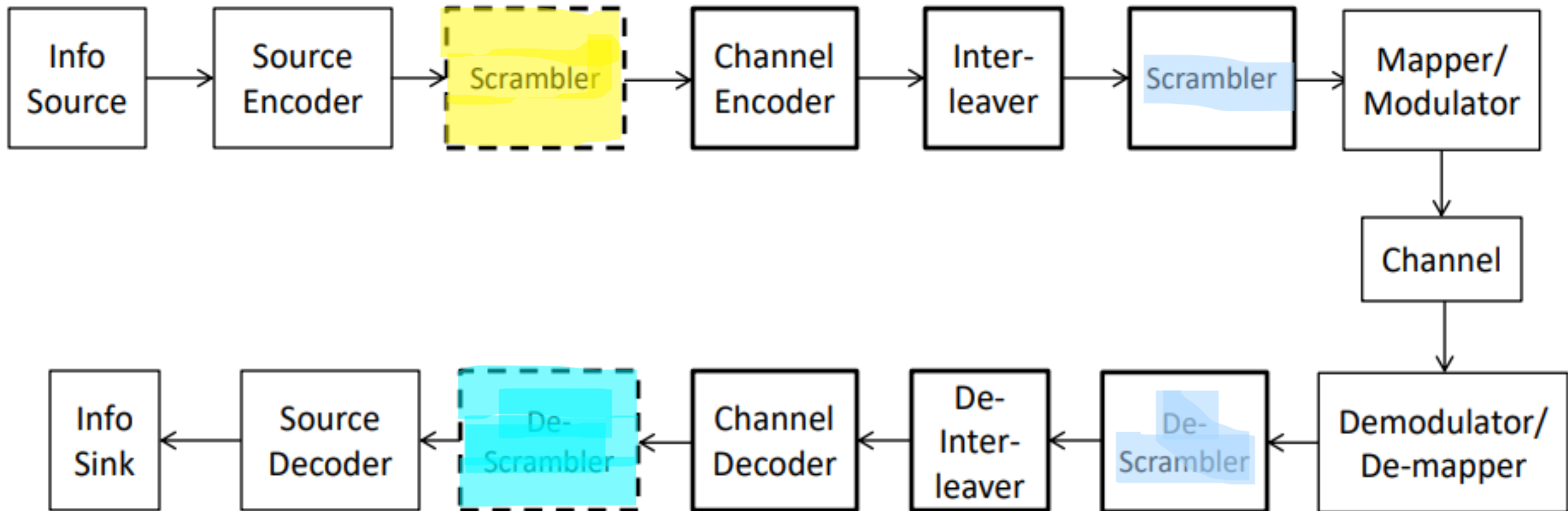

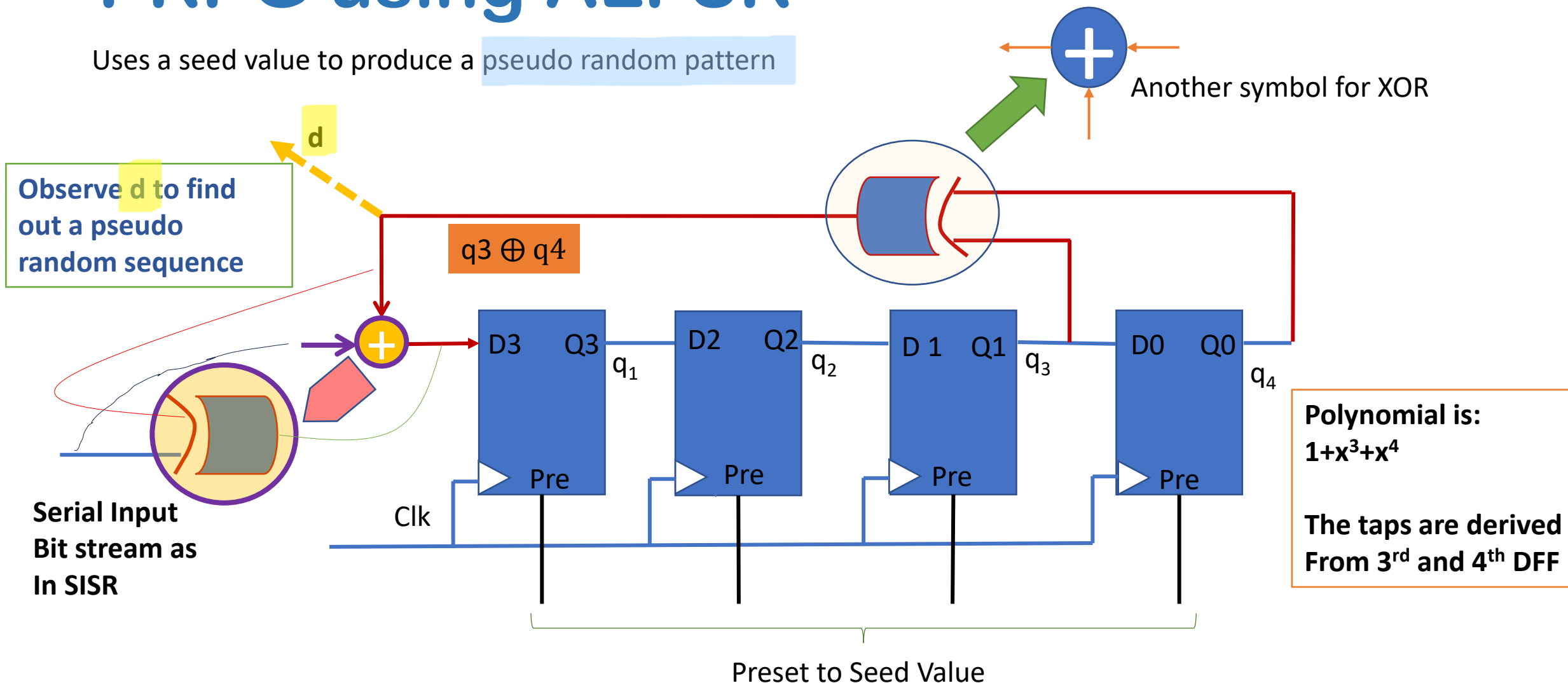
# PRPG using ALFSR

Uses a seed value to produce a pseudo random pattern





# Simplified Representation

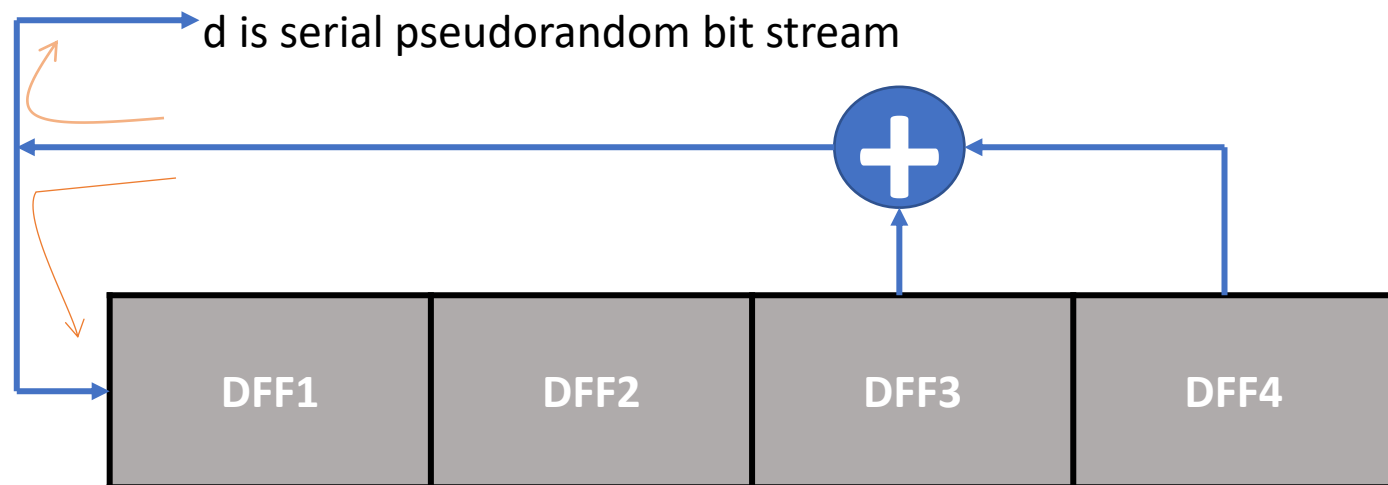

Preset

**Characteristic Polynomial**  
 $1+x^3+x^4$

The sequence observed at  $q_3q_2q_1q_0 =$   
 $\{15, 7, 3, 1, 8, 4, 2, 9, 12, 6, 11, 5, 10, 13, 14, 15, \dots\}$

q1	q2	q3	q4	d
1	1	1	1	0
0	1	1	1	0
0	0	1	1	0
0	0	0	1	1
1	0	0	0	0
0	1	0	0	0
0	0	1	0	1
1	0	0	1	1
1	1	0	0	0
0	1	1	0	1
1	0	1	1	0
0	1	0	1	1
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

# Changing seed value with same polynomial

## Question:

What happens when seed value is changed from '1111' to '1000'?

## Answer:

With seed value of '1111'

The sequence observed at  $q_3q_2q_1q_0 = \{15, 7, 3, 1, 8, 4, 2, 9, 12, 6, 11, 5, 10, 13, 14, 15, \dots\}$

With seed value of '1000'

The sequence observed at  $q_3q_2q_1q_0 = \{8, 4, 2, 9, 12, 6, 11, 5, 10, 13, 14, 15, 7, 3, 1, 8, \dots\}$

Both sequences are equal in a circle, just the starting point is different


# PRPG Cycle length vs Register length

# of Bits	Length of Loop	Taps
2	3 *	[0,1]
3	7 *	[0,2]
4	15	[0,3]
5	31 *	[1,4]
6	63	[0,5]
7	127 *	[0,6]
8	255	[1,2,3,7]
9	511	[3,8]
10	1,023	[2,9]
11	2,047	[1,10]
12	4,095	[0,3,5,11]
13	8,191 *	[0,2,3,12]
14	16,383	[0,2,4,13]
15	32,767	[0,14]
16	65,535	[1,2,4,15]
17	131,071 *	[2,16]
18	262,143	[6,17]
19	524,287 *	[0,1,4,18]
20	1,048,575	[2,19]
21	2,097,151	[1,20]
22	4,194,303	[0,21]
23	8,388,607	[4,22]
24	16,777,215	[0,2,3,23]
25	33,554,431	[2,24]
26	67,108,863	[0,1,5,25]
27	134,217,727	[0,1,4,26]
28	268,435,455	[2,27]
29	536,870,911	[1,28]
30	1,073,741,823	[0,3,5,29]
31	2,147,483,647 *	[2,30]
32	4,294,967,295	[1,5,6,31]


# Additive Scrambler and Descrambler

- **Synchronous scramblers** because they require the initial state of the scrambler and descrambler to be the same
- They are **non-recursive** because they do not have any feedback loop in the process
- LFSR is connected to the data stream by means of an additional modulo-2 adder (XOR) gate
- Used in 100Base-TX interface which repeats its sequence after  $2^N - 1 = 2047$  bits; with  $N=11$
- Usually employed where a fixed size frame is to be transmitted

# Additive Scrambler Eg. from Web

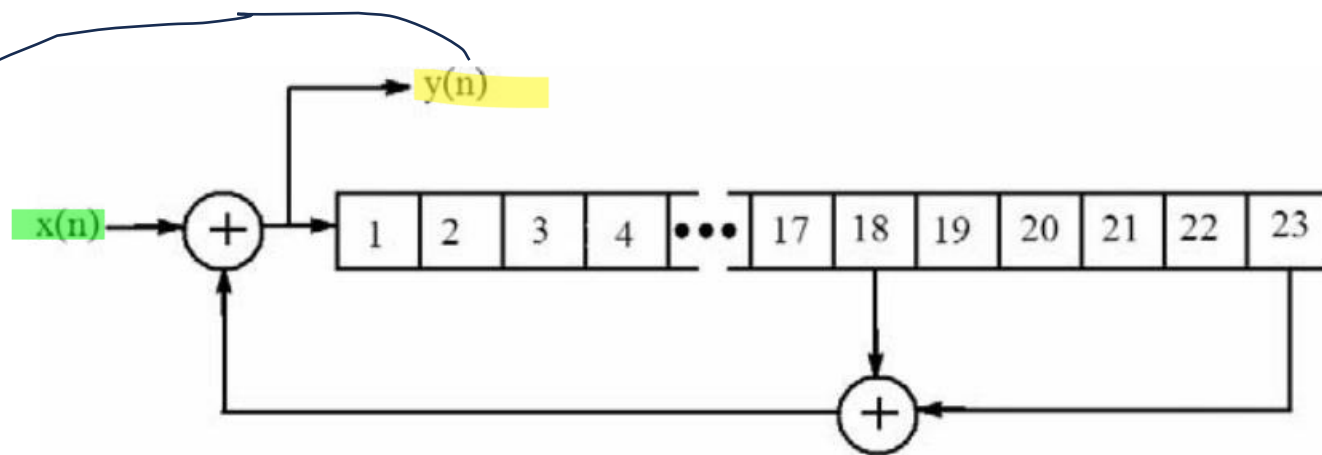


(a) scrambler

 


(b) descrambler

# Additive Scrambler Example

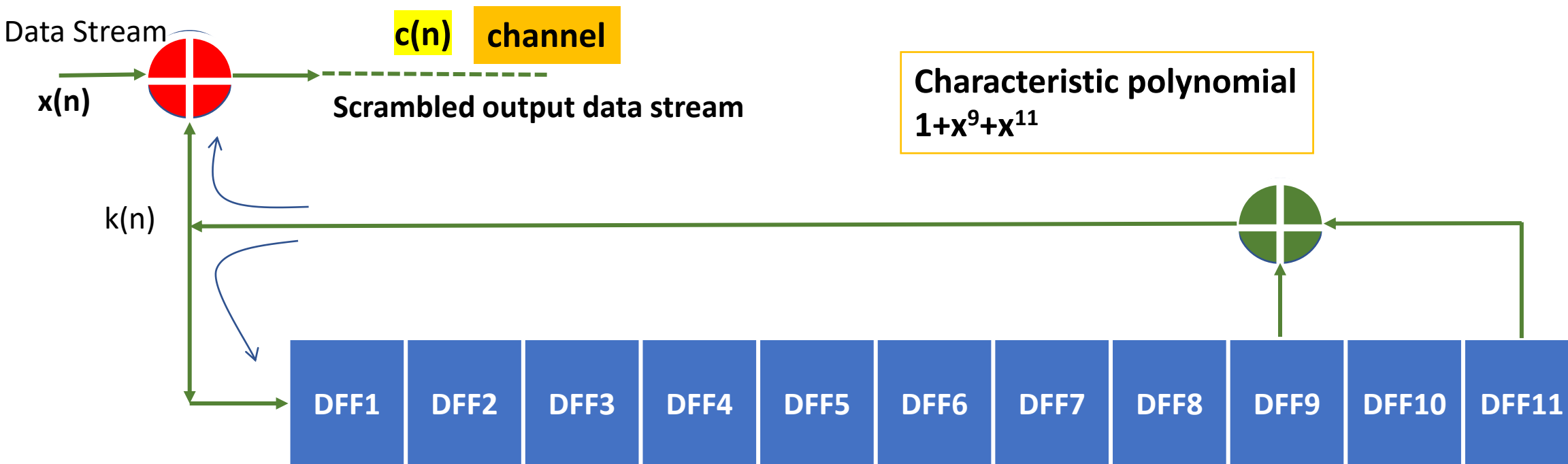

$x(n)$  represents the data to be scrambled at time  $n$   
 $k(n)$  represents the 'key' produced by the LFSR  
 $c(n)$  represents the scrambled code word

# Corresponding Additive Descrambler

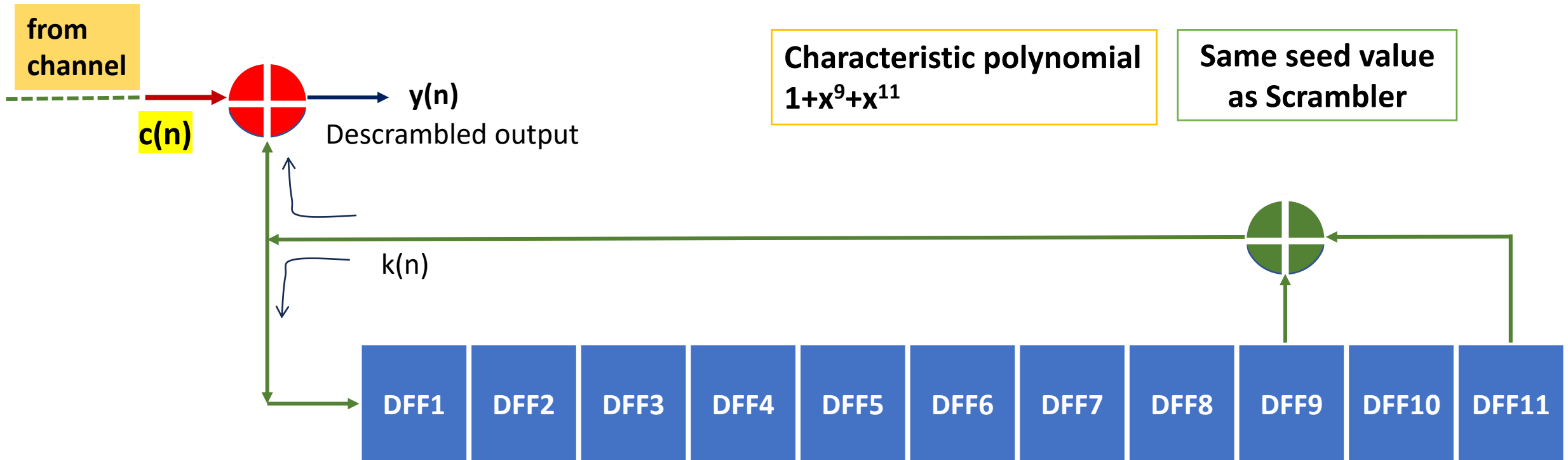


$y(n)$  represents the data de-scrambled at time  $n$   
 $k(n)$  represents the 'key' produced by the LFSR  
 $c(n)$  represents the scrambled code word

# Multiplicative Scramblers


- They are **Asynchronous** because they do not require LFSR synchronization.
- They are **recursive** as they have feedback loops.
- The pair of scrambler-descrambler is **self-synchronizing**. They do not need to start from same initial value.
- The **self-synchronizing process could take up to N bits** (or N clock cycles) so the first N values of  $y(n)$  should be discarded.
- With this approach, the transmission errors are multiplied by  $T+1$ , where T is the number of taps used in LFSR. **Thus if one bit is flipped due to some error, the descrambler will result in 3 bit error.**



# Multiplicative Scrambler - Descrambler

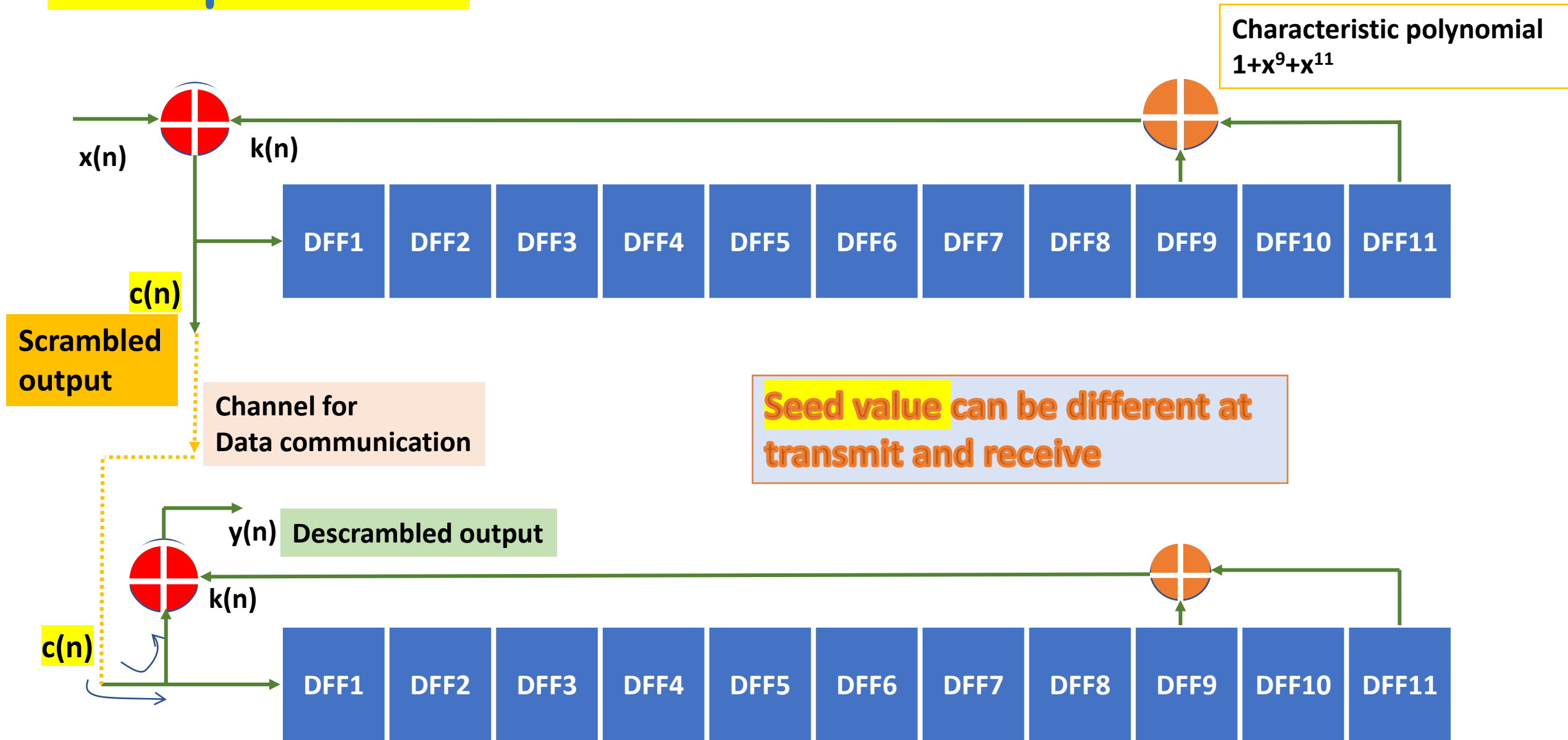


# Example – Multiplicative Scrambler

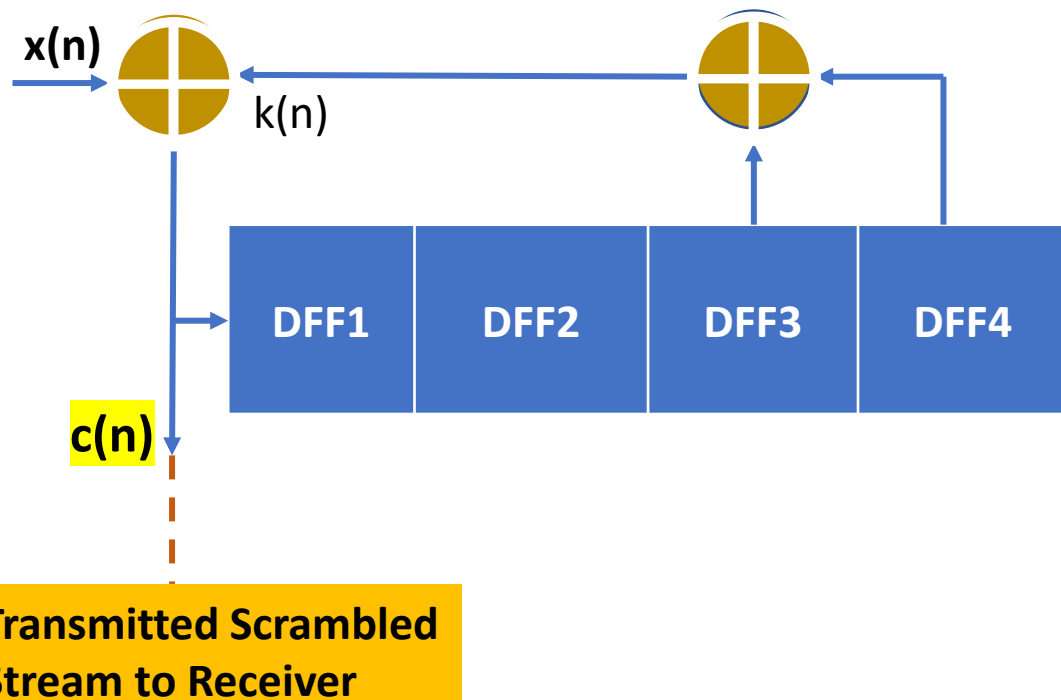

LFSR Using polynomial  $1 + x^3 + x^4$   
 Scrambler Seed Value "0000"  
 Input Data stream:  
 "101100010110"

Registers output "q1q2q3q4"				k	x	c
0	0	0	0	0	1	1
1	0	0	0	0	0	0
0	1	0	0	0	1	1
1	0	1	0	1	1	0
0	1	0	1	1	0	1
1	0	1	0	1	0	1
1	1	0	1	1	0	1
1	1	1	0	1	1	0
0	1	1	1	0	0	0
0	0	1	1	0	1	1
1	0	0	1	1	1	0
0	1	0	0	0	0	0
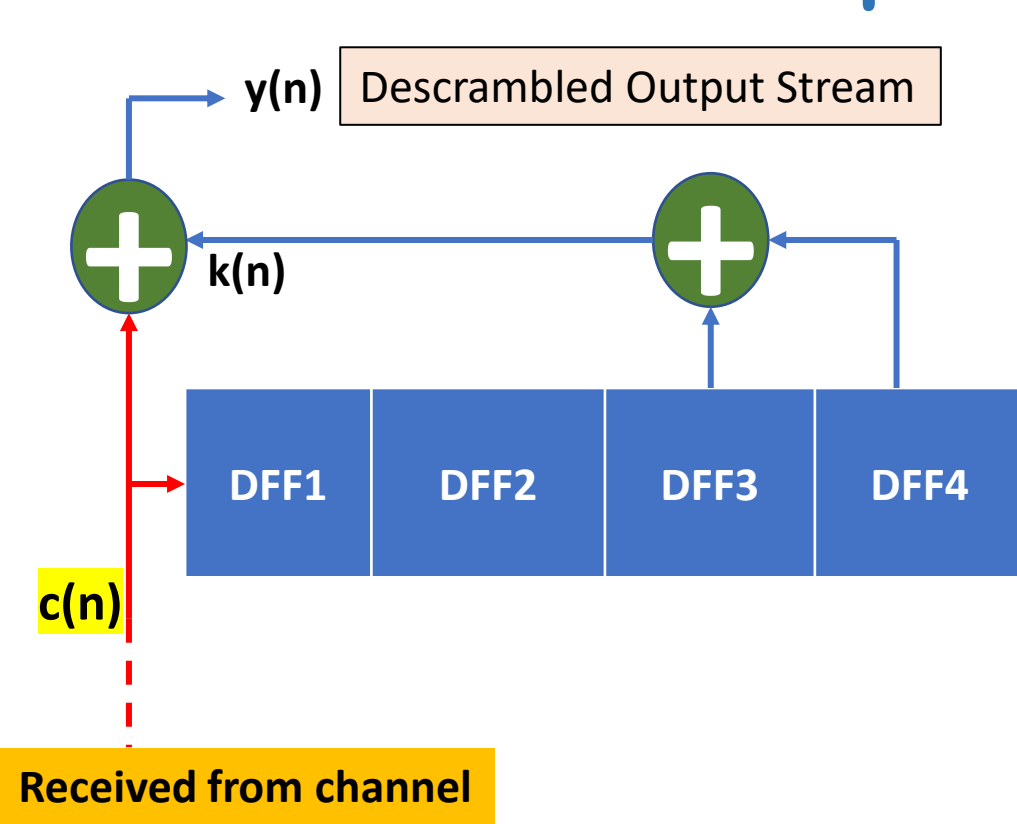
# Continue to – Multiplicative De-Scrambler



Seed


Registers output "q1q2q3q4"				k	c	y
1	1	1	1	0	1	1
1	1	1	1	0	0	0
0	1	1	1	0	1	1
1	0	1	1	0	0	0
0	1	0	1	1	1	0
1	0	1	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	0	1
0	1	1	1	0	0	0
0	0	1	1	0	1	1
1	0	0	1	1	0	1
0	1	0	0	0	0	0

N=4

y=x  
Input String From here

LFSR Using polynomial  $1 + x^3 + x^4$   
 Scrambler Seed Value "0000"  
 De-Scrambler Seed Value "1111"  
 Input Data stream:  
 "101100010110"
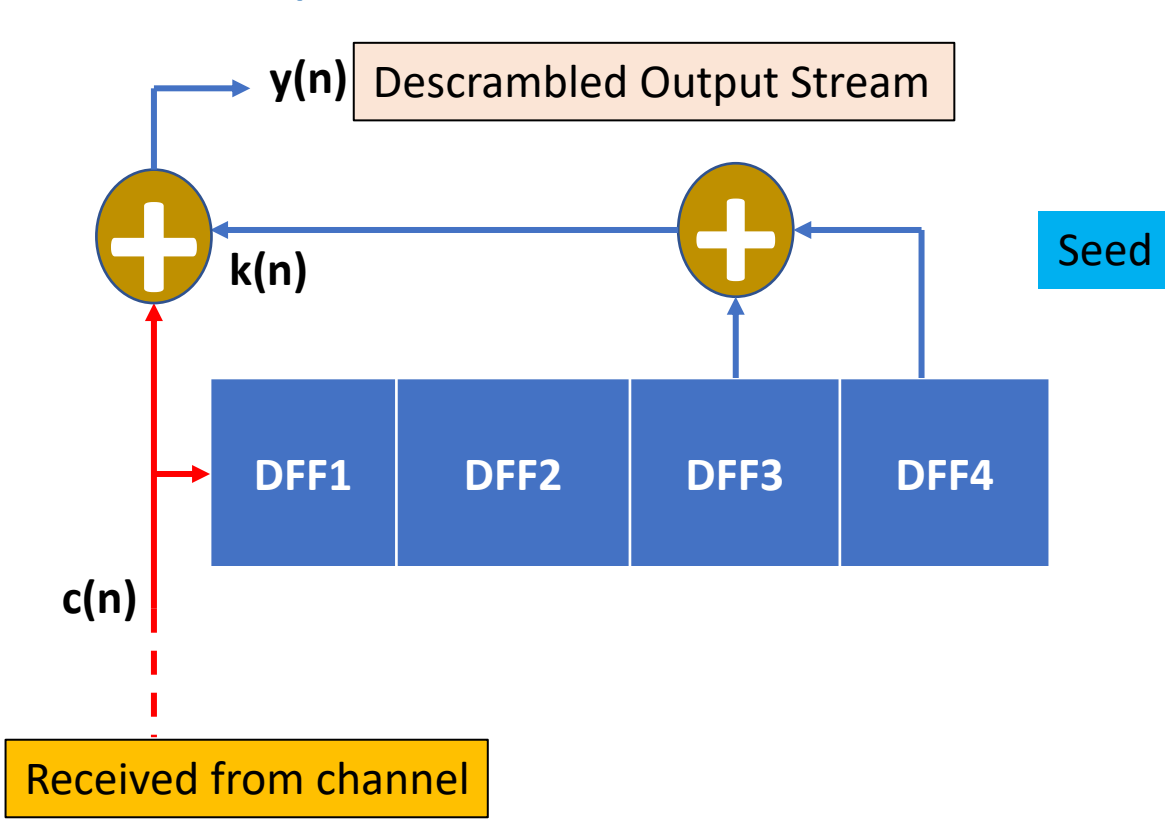
# Multiplicative De-Scrambler with Error Detection



LFSR Using polynomial  $1 + x^3 + x^4$   
 Scrambler Seed Value "0000"  
 De-Scrambler Seed Value "1111"  
 Input Data stream:  
 "101100010110"  
 T is the number of TAPS used in ALFSR

Registers output "q1q2q3q4"				k	c	y	N=4
1	1	1	1	0	1	1	
1	1	1	1	0	0	0	
0	1	1	1	0	1	1	
1	0	1	1	0	0	0	y=x Input String From here
0	1	0	1	1	1	0	
1	0	1	0	1	0	1	
1	1	0	1	1	1	0	
1	1	1	0	1	0	1	
0	1	1	1	0	0	1	
0	0	1	1	0	1	0	
1	0	0	1	1	0	1	
0	1	0	0	0	0	0	
1	1	1	1	1	1	1	
1	1	1	1	1	1	1	
1	1	1	1	1	1	1	

One error in blue was introduced in  $c(n)$   
 This error resulted in  $T+1 = 3$  errors in  $y(n)$  shown in red

# Case Study: Binary Rate Multipliers



# Binary Rate Multipliers - BRM

**Definition: A circuit module that transforms a stream of input clock pulses into another stream of output clock pulses**

Let  $N_i$  = no. of input pulses for a particular time period

Let  $N_o$  = no. of output clock pulses for the same time period

***Binary Fractional Rate Multiplier***  $\Rightarrow N_o = \frac{B}{2^n} N_i$

$B$  = Rate Constant Input to module

$$B = (B_{n-1}, B_{n-2}, \dots, B_2, B_1, B_0)_2$$

$n$  = no. of binary counter stages controlling the module

The clock input drives an  $n$ -bit binary counter whose outputs are labelled  $(X_n, X_{n-1}, \dots, X_2, X_1)$ .

Will do next lecture due to quiz today