

Lecture 18

EE 421 / CS 425

Digital System Design

Fall 2025

Shahid Masud

Topics

- Floating Point Adder and Multiplier Operation (quick recap)
- Digital Circuit Design for Floating Point Module
- Introduction to Programmable Logic Hardware Device
- Nomenclature and types
- Logic Array Circuits
- PLA and PAL
- Programmable Logic Devices – PLD

Floating Point Arithmetic – Digital Design


$$N = (-1)^S \times (1+F) \times 2^E$$

E.g. $91.820734 \times 10^{-34}$


- ❖ A signed-magnitude system for the fractional part and a biased notation for the exponent
- ❖ Three subfields
 - ❖ Sign S
 - ❖ Fraction F (or Significand or Mantissa)
 - ❖ Exponent E
- ❖ Sign bit is 0 for positive numbers, 1 for negative numbers
- ❖ Fractions always start from **1**.xxxx, hence the integer **1** is not written (register has xxxx)
- ❖ Exponent is biased by +127 (add 127 to whatever is in register bits)
- ❖ Normalize: Express numbers in the standard format by shifting of bits and adding / subtracting from Exponent register

IEEE 754 Floating Point Representation

Single Precision IEEE 754

 

Double Precision IEEE 754

 

Examples of Floating Point Representation

$-(13.45)_{10}$
 $= (1101.01\ 1100\ 1100\ 1100\ \dots)^2$; this is un-normalized
 $= (1.10101\ 1100\ 1100\ 1100\ 1) \times 2^3$; normalized
 Fraction part is 10101 1100 1100 1100 1
 Biased Exponent is $3+127 = 130$
 Sign = 1

5.0345
 $= 101.0000\ 1000\ 1101\ 0100\ 1111\ 110$; this is un-normalized
 $= 1.01\ 0000\ 1000\ 1101\ 0100\ 1111\ 110 \times 2^2$; normalized
 Biased Exponent = $2+127 = 129 = (1000\ 0001)_2$
 Fraction = 01 0000 1000 1101 0100 1111 110
 Sign = 0

Floating Point Arithmetic – Digital Design

$$N = (-1)^S \times (1+F) \times 2^E$$

E.g. $91.820734 \times 10^{-34}$

- ❖ A signed-magnitude system for the fractional part and a biased notation for the exponent
- ❖ Three subfields
 - ❖ Sign S
 - ❖ Fraction F (or Significand or Mantissa)
 - ❖ Exponent E
- ❖ Sign bit is 0 for positive numbers, 1 for negative numbers
- ❖ Fractions always start from **1**.xxxx, hence the integer **1** is not written (register has xxxx)
- ❖ Exponent is biased by +127 (add 127 to whatever is in register bits)
- ❖ Normalize: Express numbers in the standard format by shifting of bits and adding / subtracting from Exponent register

Floating Point Multiplication

Consider two floating point numbers:
 $(F_1 \times 2^{E1})$ and $(F_2 \times 2^{E2})$

Denormalize

The product of these two numbers is:

$$= (F_1 \times 2^{E1}) \times (F_2 \times 2^{E2})$$


$$= (F_1 \times F_2) \times 2^{(E1+E2)}$$

$$= F \times 2^E$$

Sign of result depends on Sign of the two numbers

Normalize

Data Path of Floating Point Multiplier

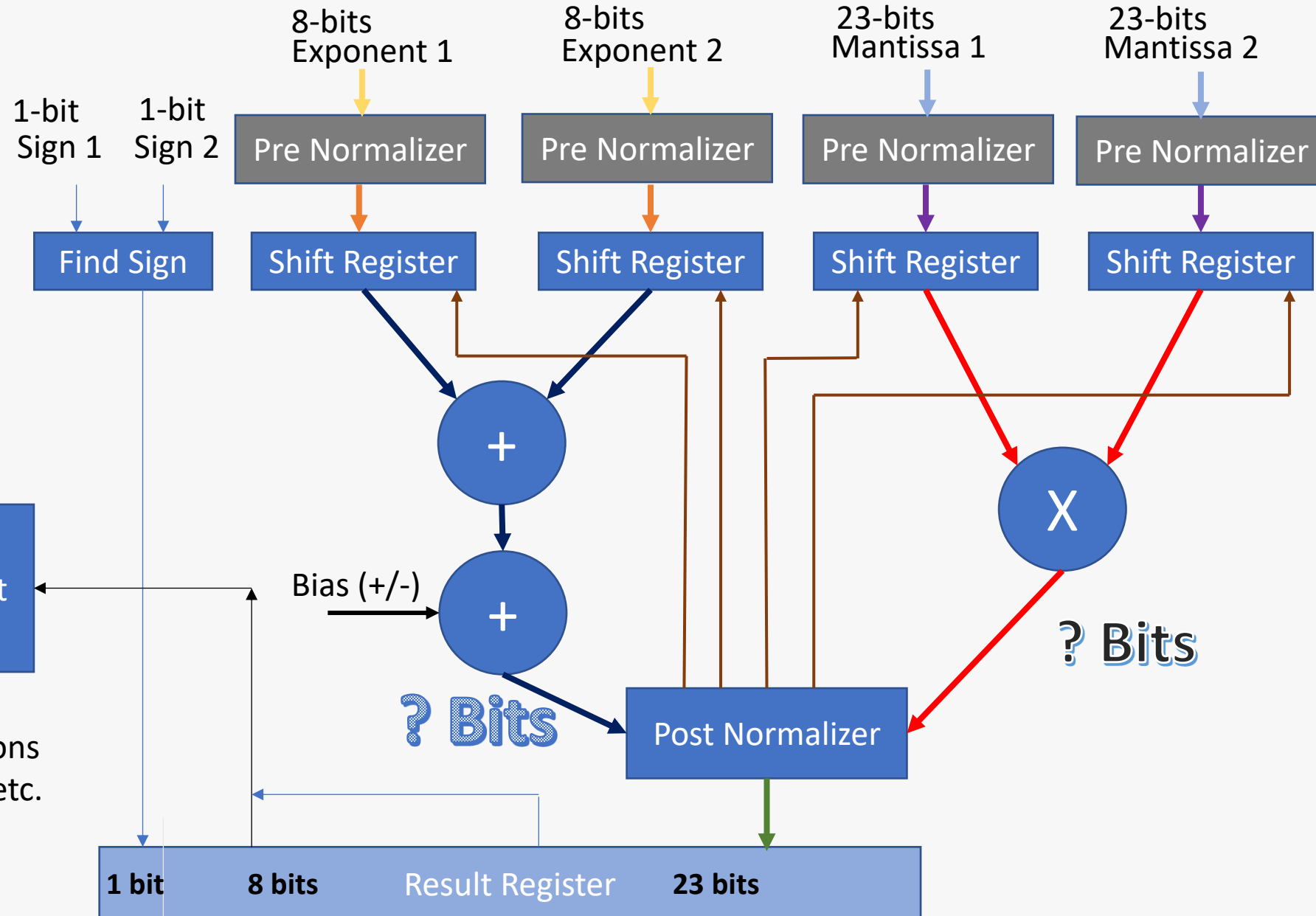

Floating Point Addition

Consider two floating point numbers:
 $(F_1 \times 2^{E1})$ and $(F_2 \times 2^{E2})$

Initial Denormalize

The addition of these two numbers is:

$$= (F_1 + F_2) \times (2^{E_{\text{new}}})$$

E_{new} is obtained by Shl or Shr of F_1 and F_2 so that E_1 becomes same as E_2


$$= F \times 2^{E_{\text{new}}}$$

Final Normalize

Take into account Guard Bits

Sign of result depends on Sign of the two numbers

Complexity of Normalize and DeNormalize

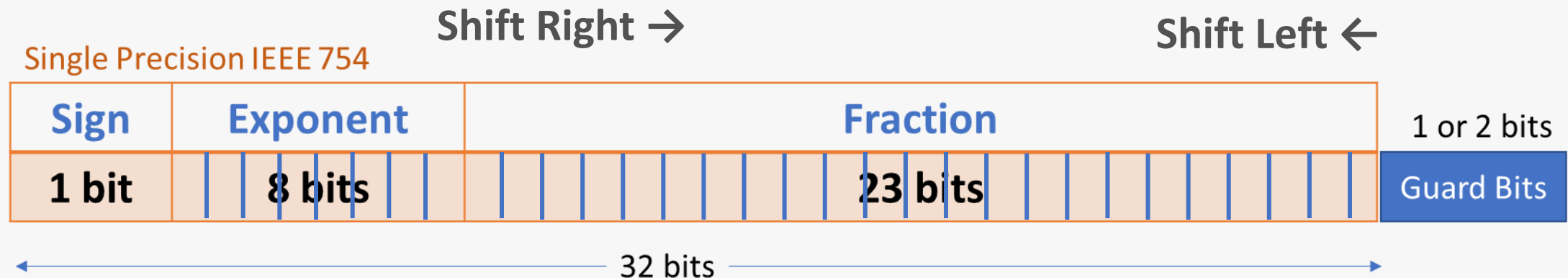

What is the Complexity, in terms of time and area?
Can this be improved?

Programmable Logic Reconfigurable Logic


Definition of Programmable Logic

- A family of semiconductor integrated circuits that can be reconfigured through:
 - special hardware-description-languages, and
 - associate Electronic Design Automation tools
 - Special configuration equipment

to produce a variety of hardware functionality from the same integrated circuit chip.

- The functionality in hardware can be erased and reconfigured in a manner analogous to design of a software system using microprocessor.
- All other types of semiconductors have fixed and pre-defined functionality.
- Performance vs Flexibility tradeoffs exist, as with any other digital system.

Programmable Logic Broad Classification

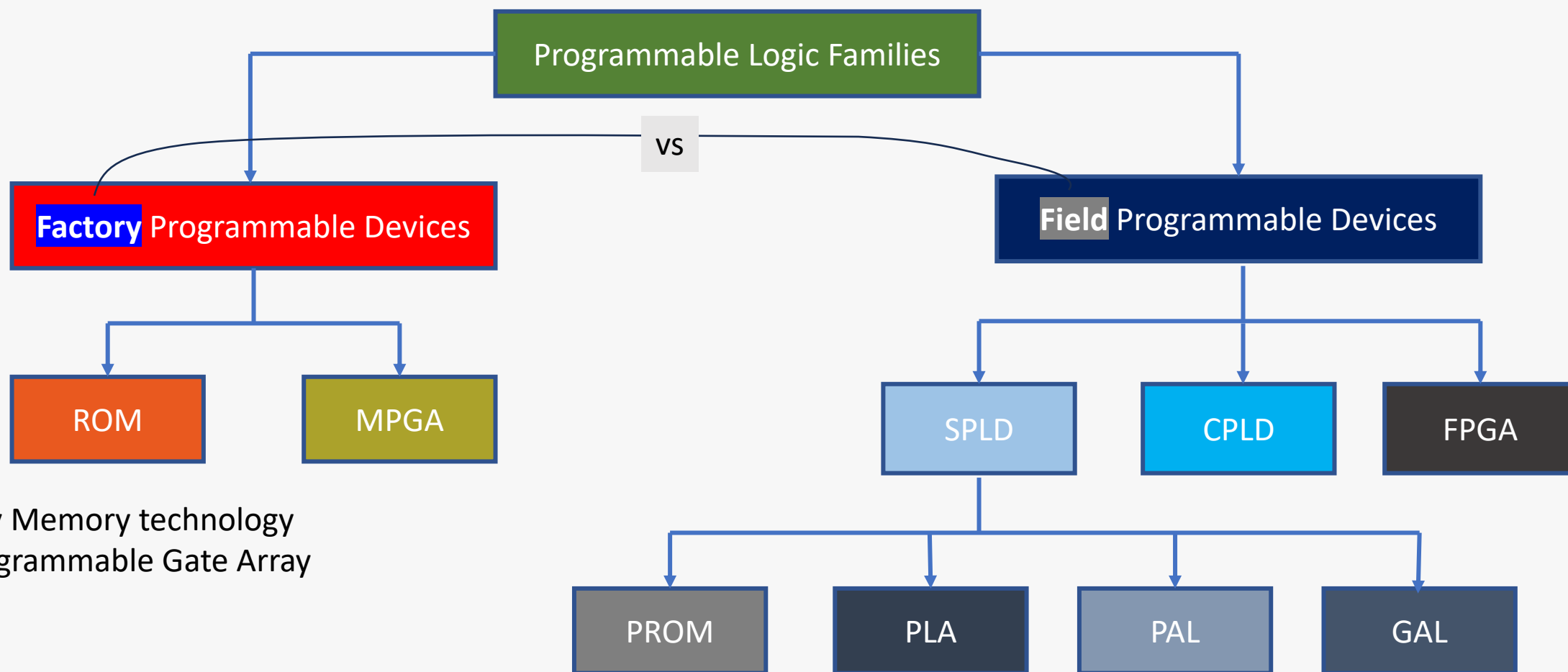

Read only Memory technology
Mask Programmable Gate Array

Simple and Complex Programmable Logic Devices

Field Programmable Gate Array

Generic Array Logic (complex PAL by lattice semi), Programmable Logic Array

Diode – Principle of operation



→ Current flow


Forward Biased



X Current flow

Reverse Biased



Diode in logic gates

 

**When A=1, Diode is Reverse Biased
Hence Output Y = 1 through +VDD**


**When A=0, Diode is Forward Biased
Hence Output Y = 0 through A = 0 Volt**

Diode based AND Logic Array

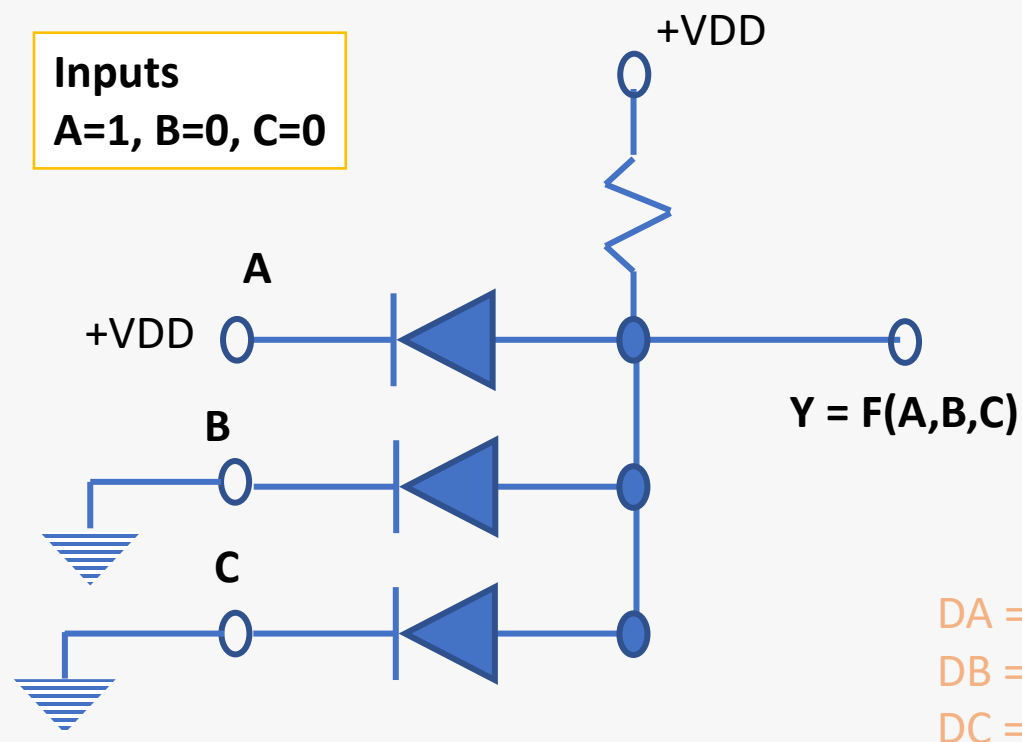 


DA=Open Circuit, DB = Forward Biased Short, DC = Forward Biased Short
Y= Logic '0' as it is Shorted to Zero due to DB or DC

Diode based OR array

 


Inputs A = 0, B = 1, C = 0

 

DA and DC = Open Circuit due to Zero input, DB = Short Circuit due to +VDD input
Y = +VDD Logic '1' due to DB being short circuit, other paths are open circuit

Diode based AND-OR Array

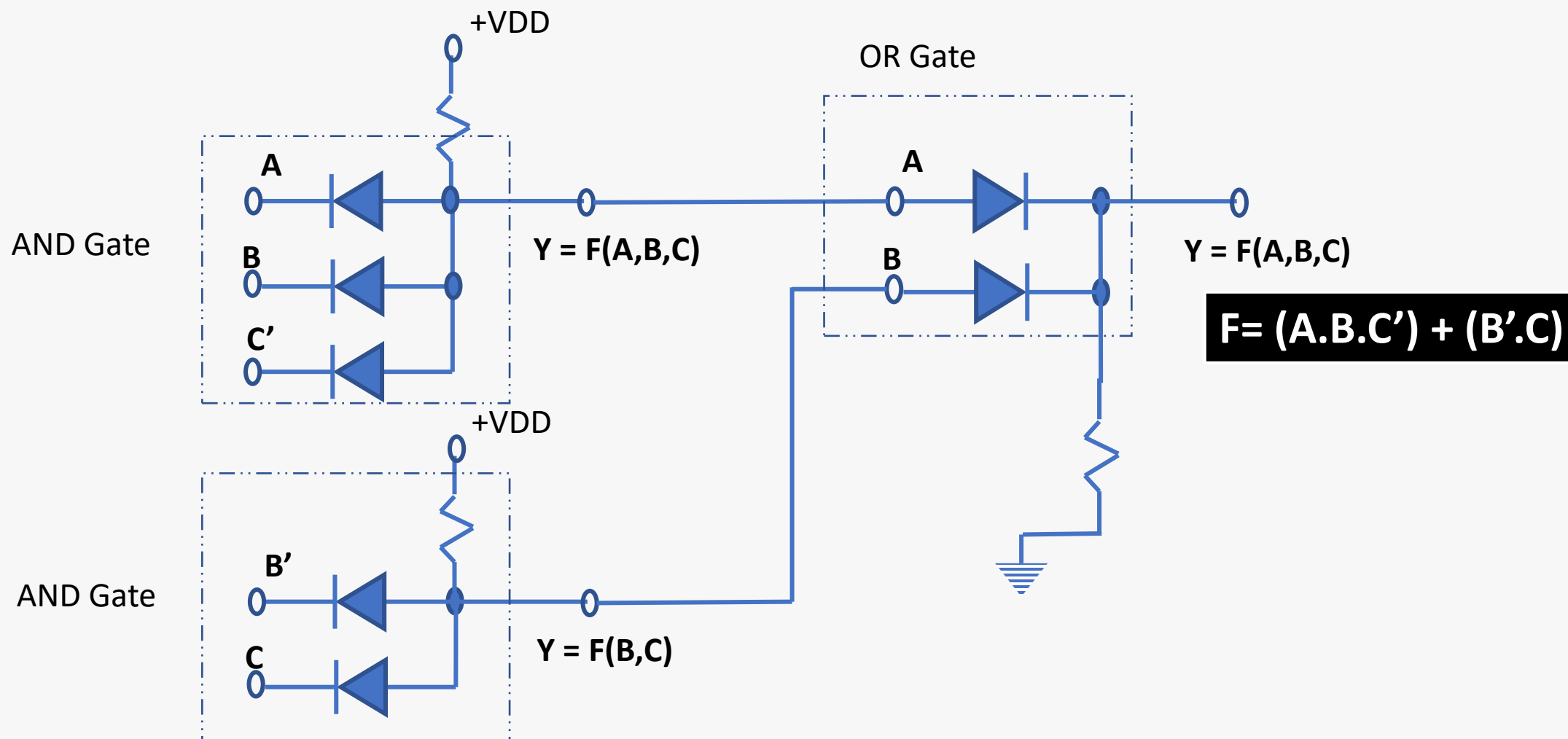

Diode as fuse


Momentarily apply a higher voltage where open circuit path is required



Desired paths from AND gates and OR gates will be retained, others will be blown out



Desired Paths are selected through a MASK during final stages of FABRICATION PROCESS

MOS Transistor as Switch

 


Programming is achieved through controlling GATE Voltage
 High GATE Voltage will ensure flow of current, like a short circuit
 Low GATE Voltage will ensure no flow of current, like an open circuit

 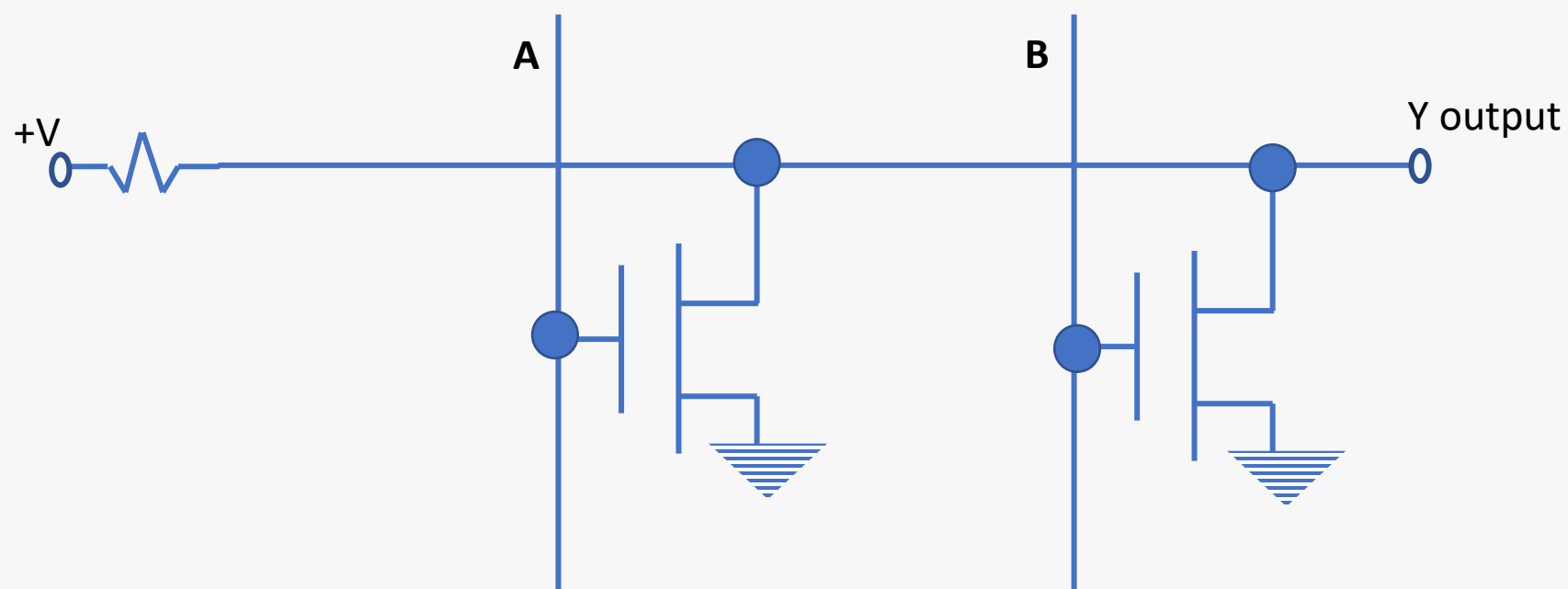Logic Gates Design with Transistor Switches



 
Transistors as Programmable Logic Switches



Different logic functions are realized through transistor switches


outputs

AND-OR Logic Array


 


PLA = Programmable
Logic Array
Comprises Programmable
AND-OR Gates

Fuse Programmable Logic Array

 



PAL – Programmable Array Logic

 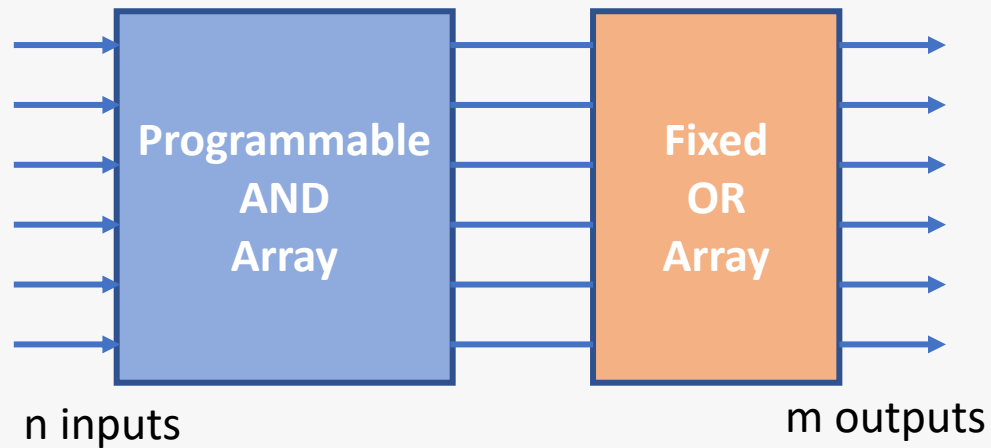

©Elprocus.com



<https://www.elprocus.com/what-are-pal-and-pla-design-and-differences/>

PLA – Programmable Logic Array

 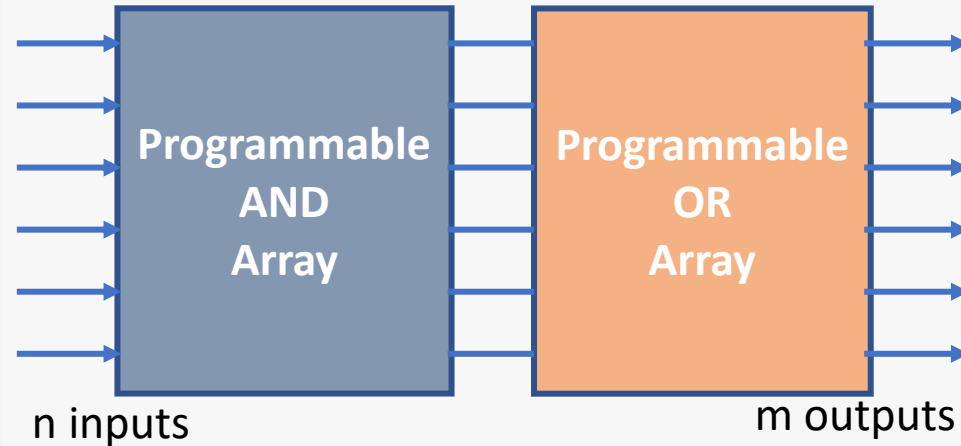


©Elprocus.com

For Exercise

 
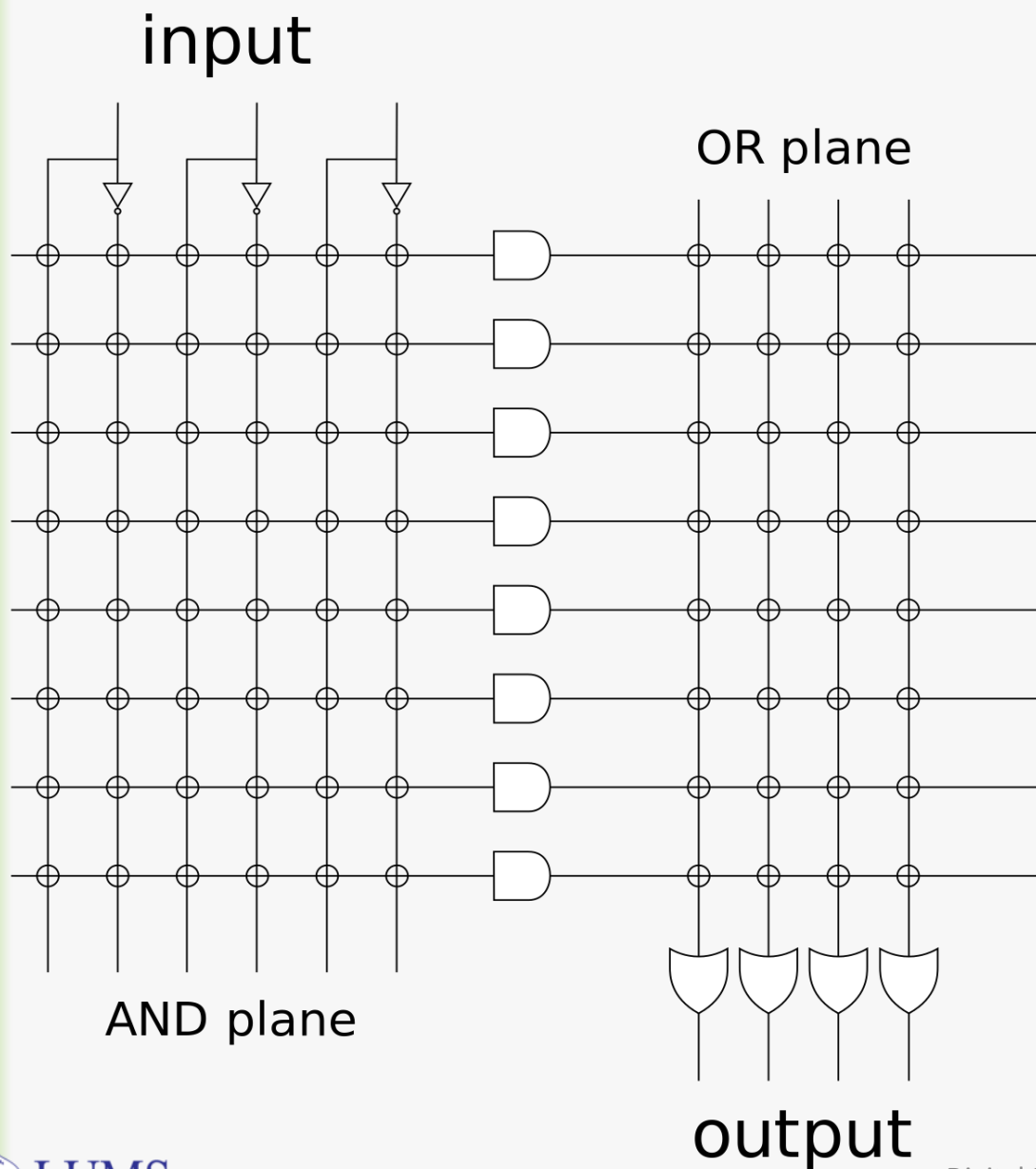


Example of PLA


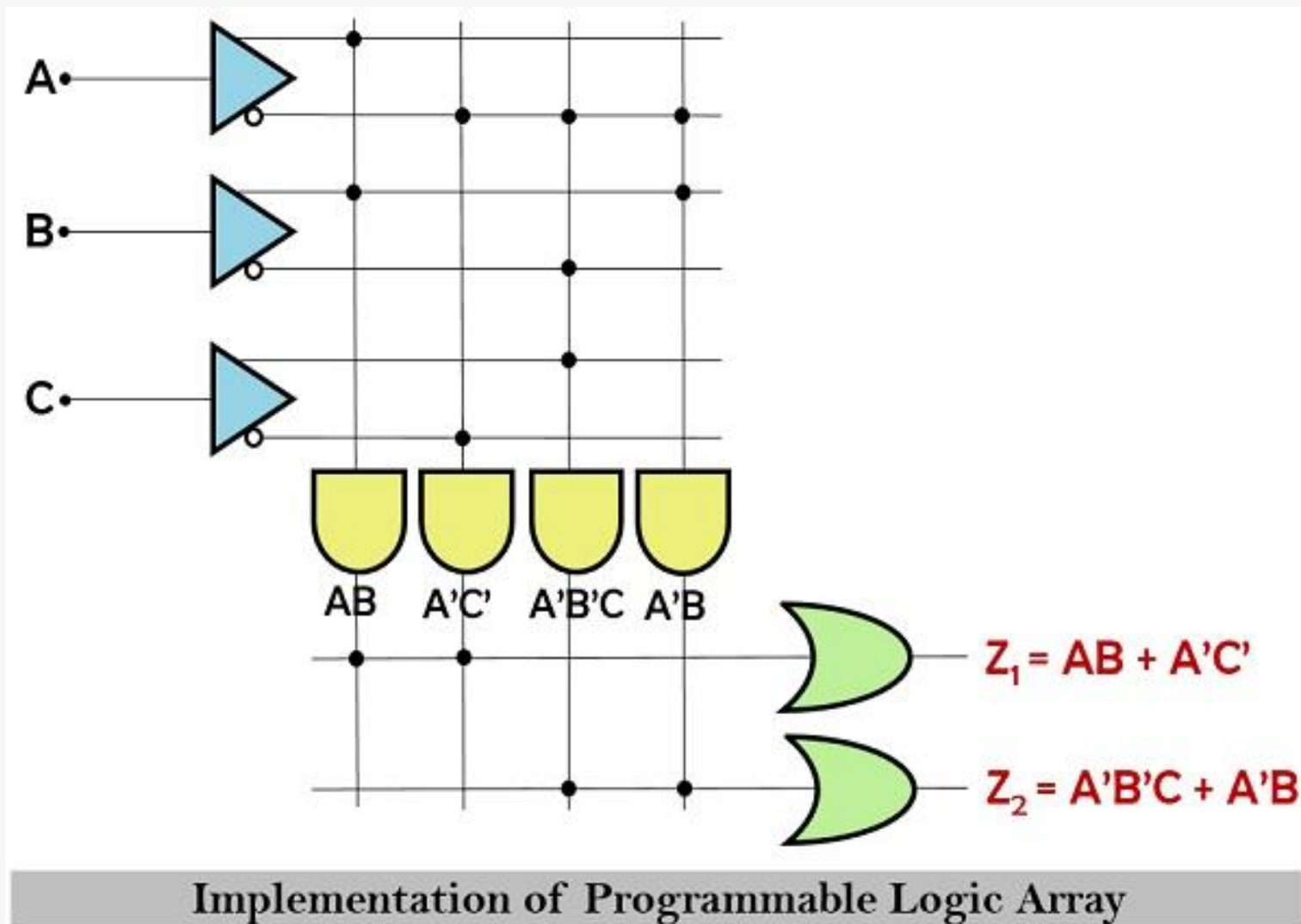


Electronics Coach

PAL – Programmable Array Logic

 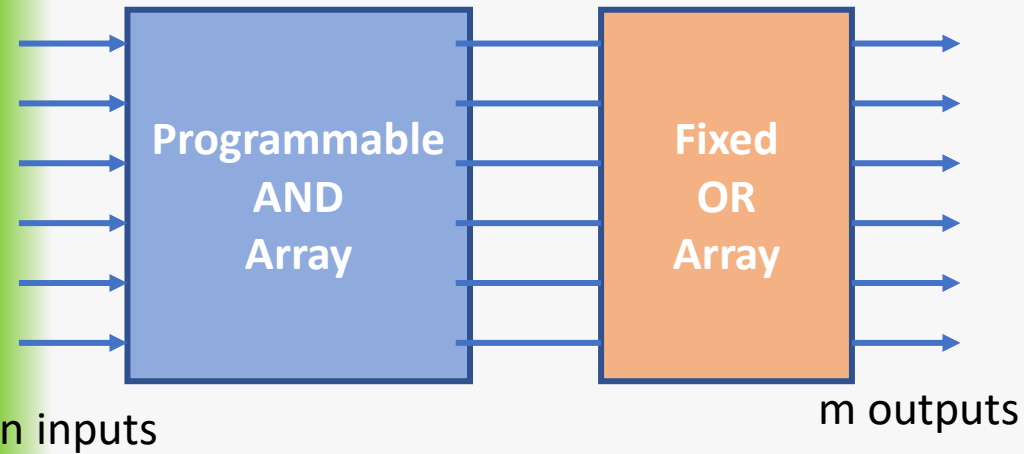


PLA – Programmable Logic Array

 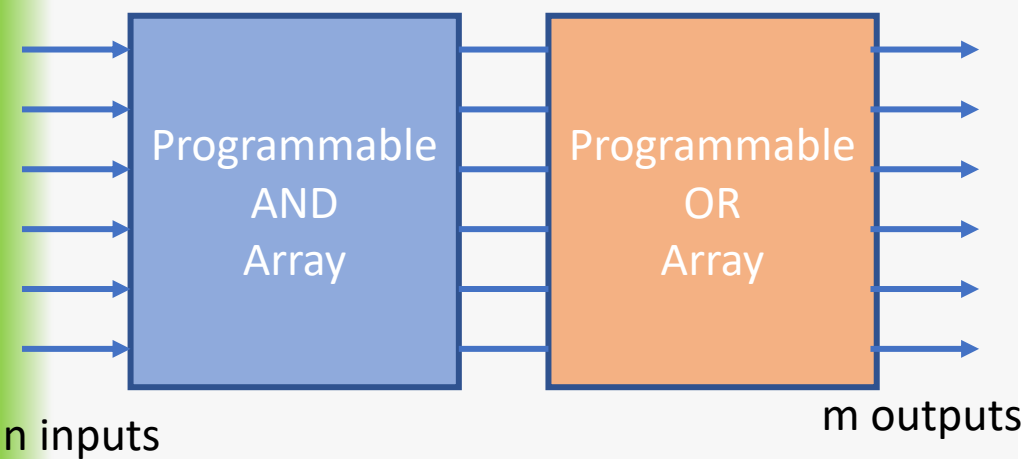


The diagram illustrates a 2D programmable logic device architecture. It consists of an **AND plane** and an **OR plane**.

- Input:** Three vertical lines at the top represent the input signals.
- AND plane:** A grid of 8 horizontal lines (AND gates) and 6 vertical lines (input lines). Each intersection is a programmable connection point (represented by a small circle). The first three vertical lines have inverters (triangles) connected to them, indicating that the first three inputs are inverted.
- OR plane:** A grid of 8 horizontal lines (OR gates) and 4 vertical lines (output lines). Each intersection is a programmable connection point (represented by a small circle).
- Output:** Four vertical lines at the bottom represent the output signals.

 


Digital System Design Lec 18 Fall 2025

Example of PLA

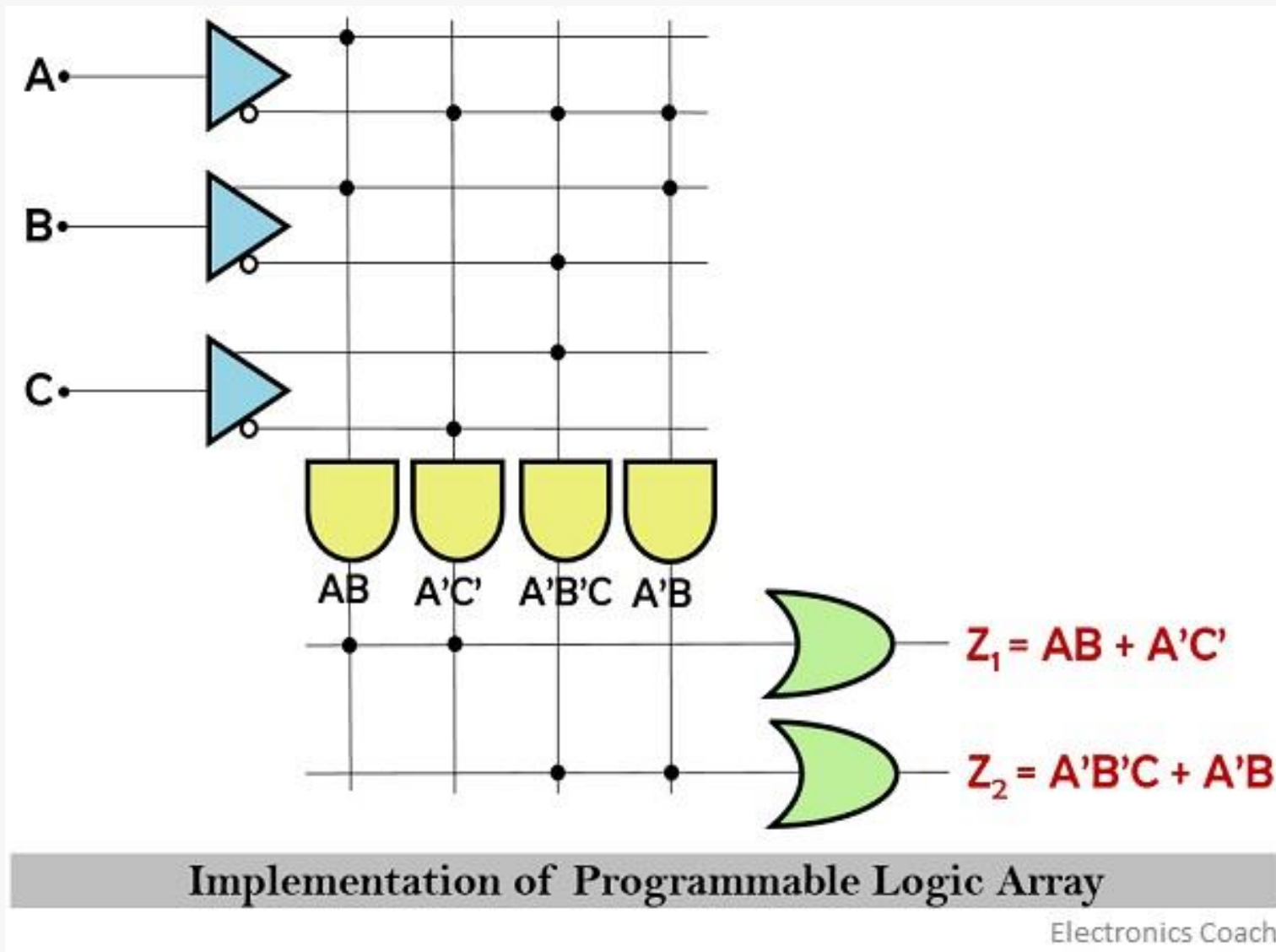

PAL – Programmable Array Logic Example

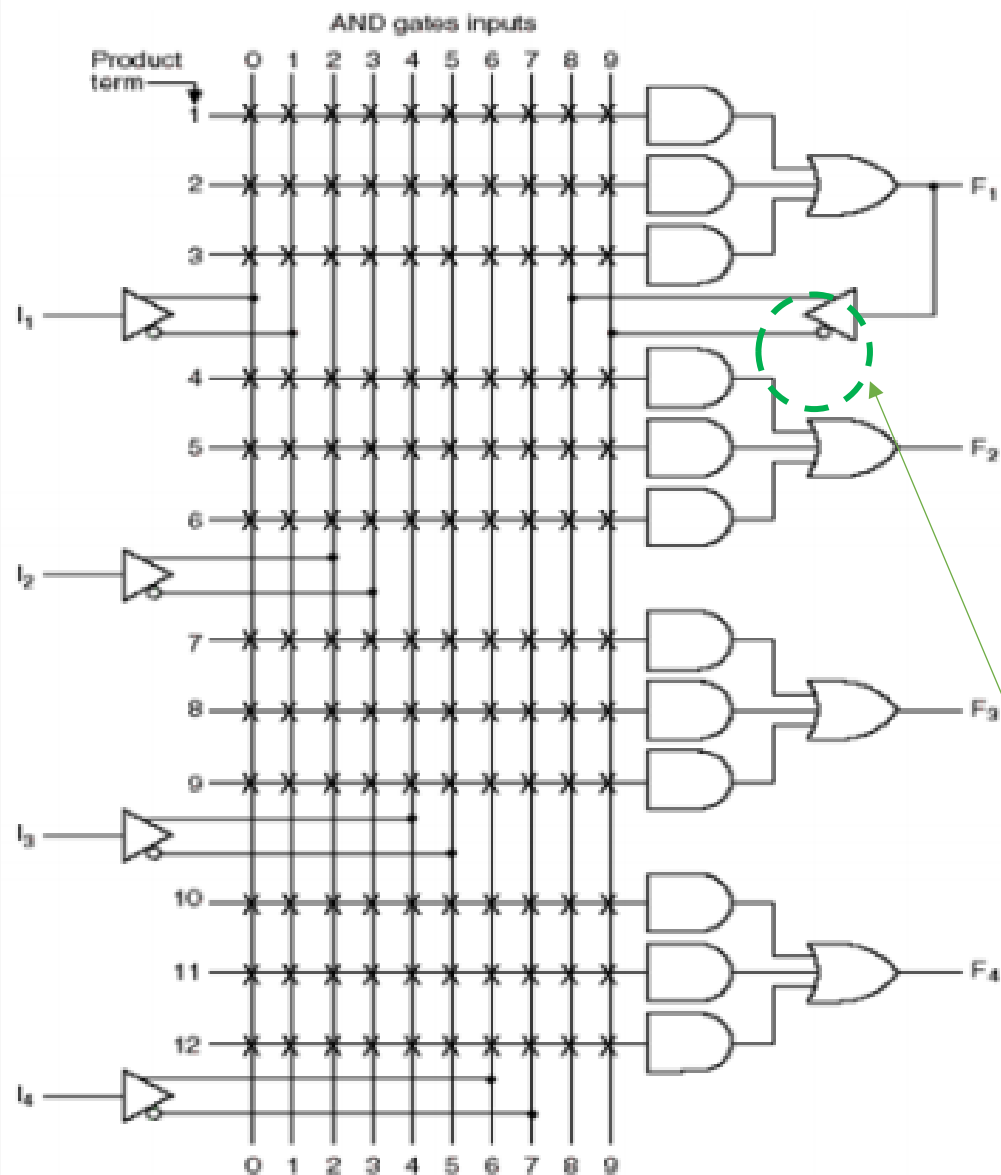


- PAL Device is a PLD with fixed OR array and a programmable AND array
- As only AND gates are programmable, PAL is easier to program but it is less flexible compared to PLA devices

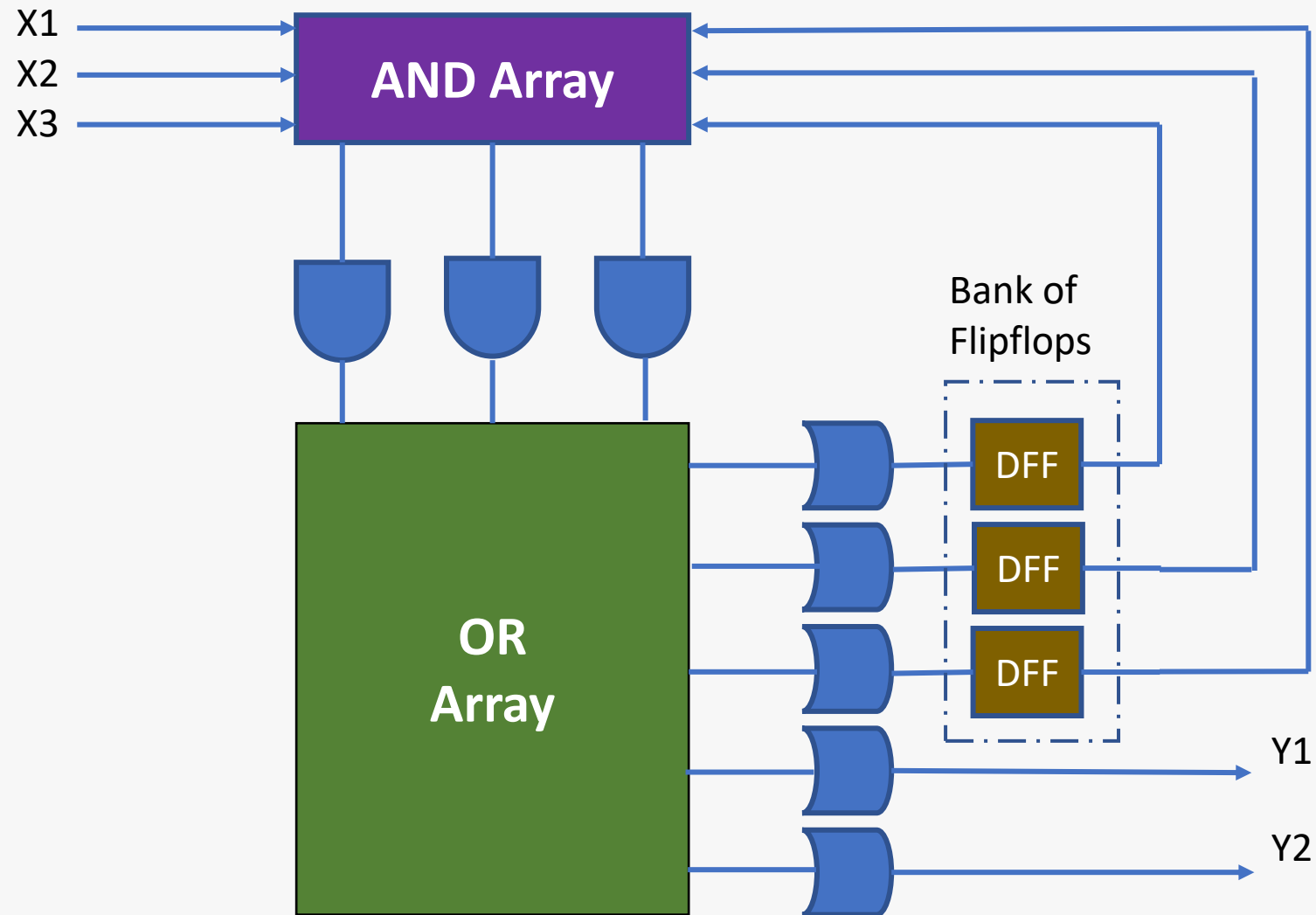
Example device:

- This device has 4 inputs and 4 outputs.
- Each input has a buffer and inverter, output is from fixed OR gate
- The device has 4 sections: Each section comprises 3 wide AND-OR array, meaning three programmable AND arrays in each section
- Each AND gates has 10 programmable input connections
- One of the outputs (see F_1) can be fed back to the inputs of AND gate through programmable connections


Sequential Circuits with PLD – Mealy Machine





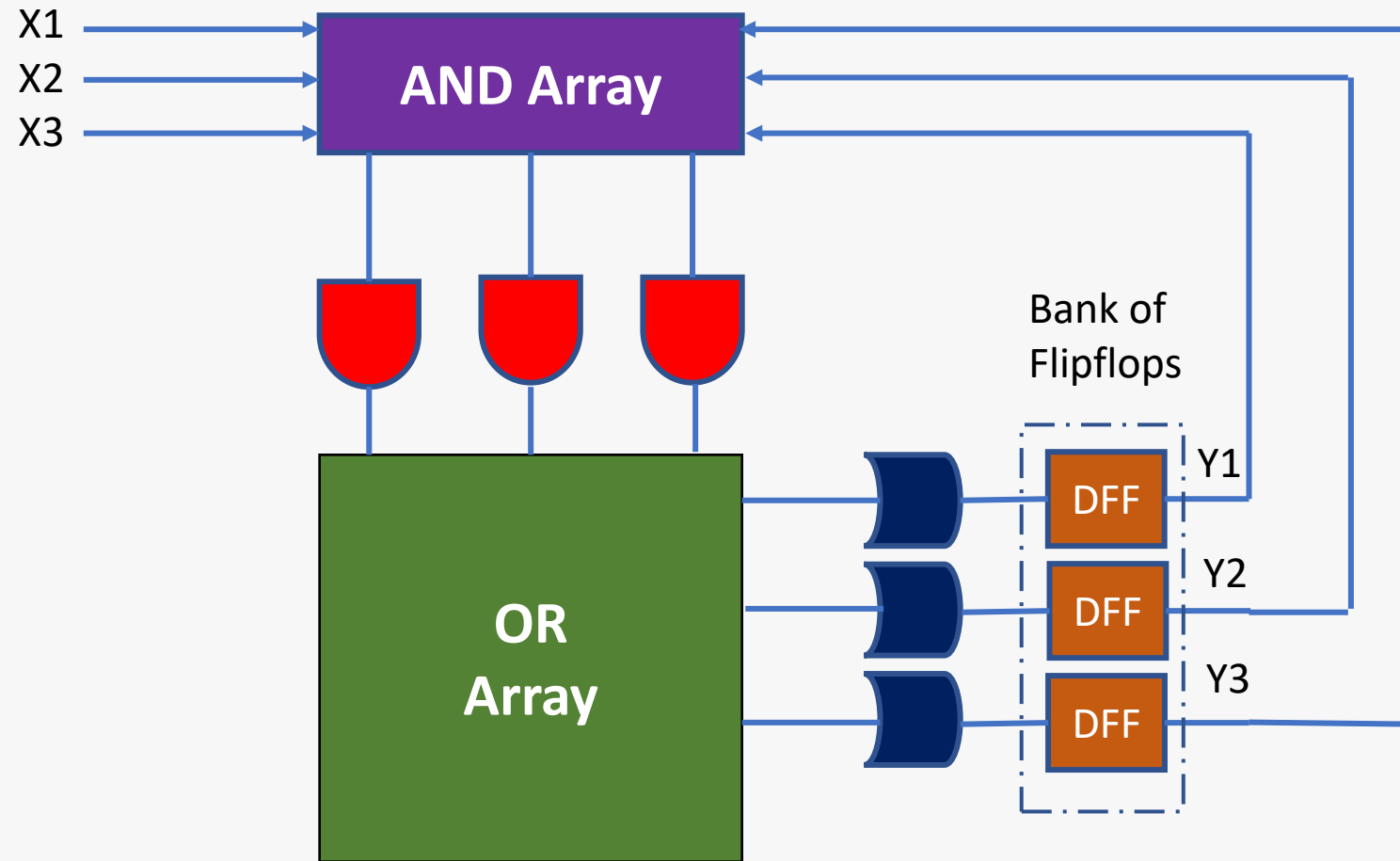
Sequential Circuits with PLD – Moore Machine



Output Polarity Control

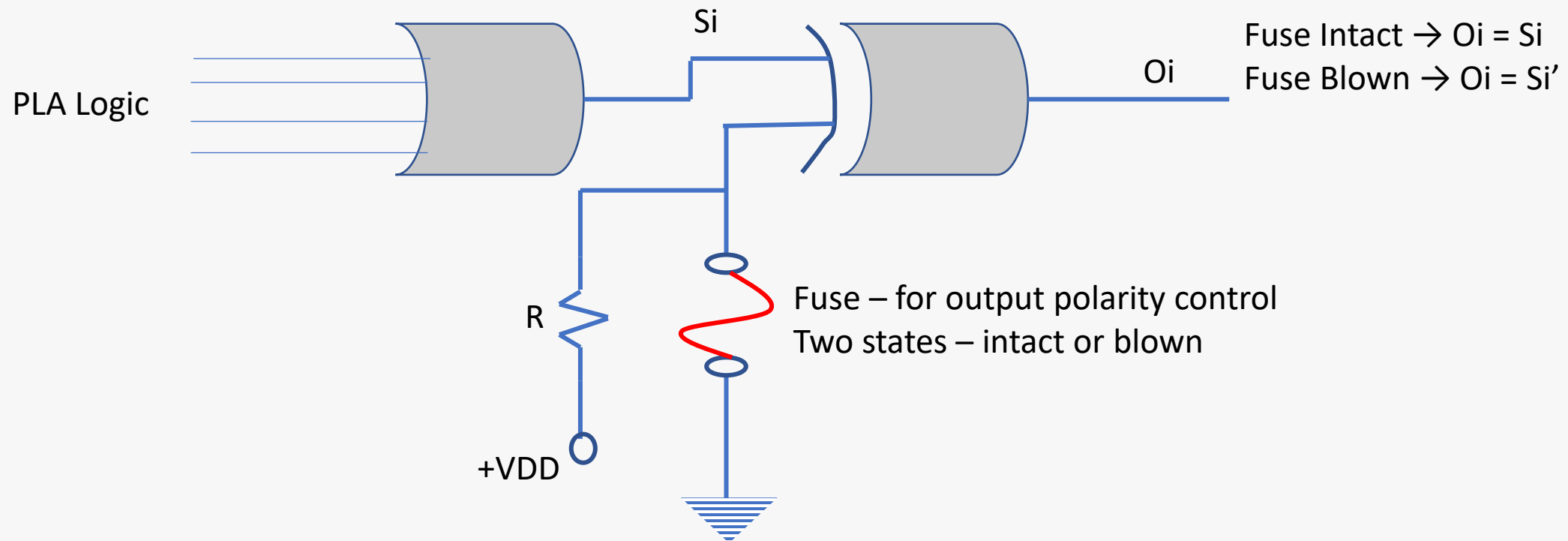

PLA Family Examples

 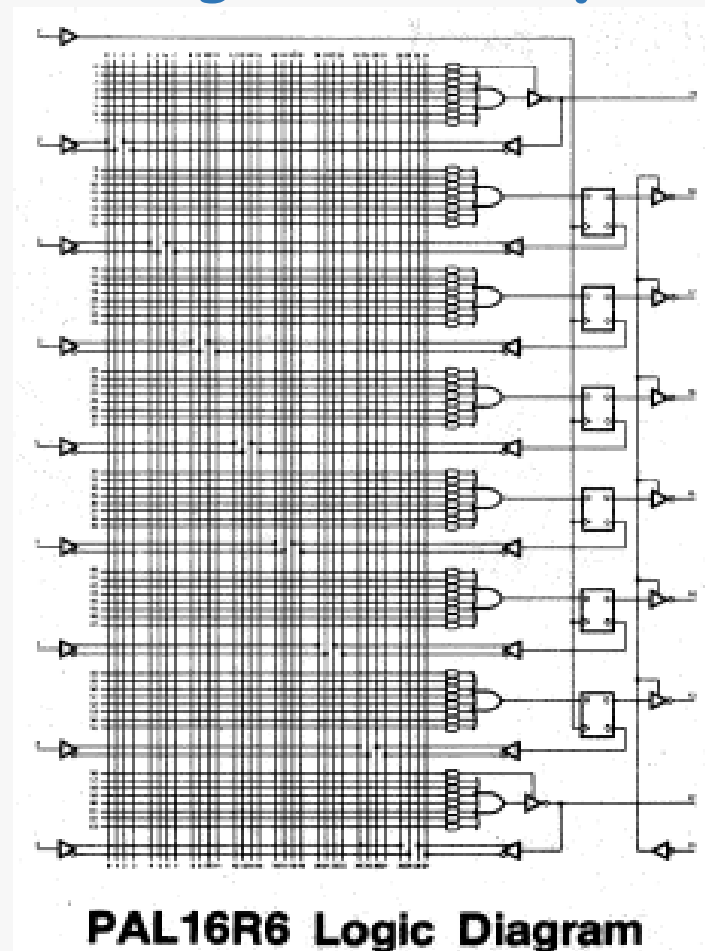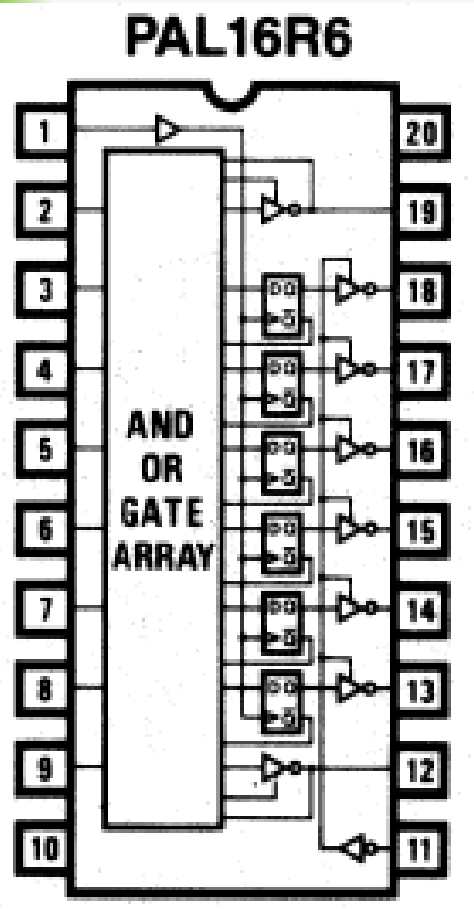

20-Pin PAL Logic Symbols

